

www.lip.pt/~pedjor/PCLD


- Combinational logic
- Modules
- Sequential Logic
- Tools

Refs:


Cyclone II device Handbook, Altera corp.
Quartus II Handbook , Altera corp.
DE2 documentation
Verilog HDL, S. Palnitkar, Prentice Hall

74LS.... vs FPGAs

Functional Specifications

 

so 2³

 

AB		00	01	11	10
0	0	0	0	1	0
0	1	1	1	1	1

$$Y = A \cdot C + B \cdot C + A \cdot B$$


We're done!



AB		11	10
0	1	1	1
1	0	0	1
1	1	1	1

$$Z = \bar{B} \cdot \bar{D} + \bar{B} \cdot C + \bar{A} \cdot C$$

gates:

 

HDL
code

Gate Level Description

Verilog has built-in basic logic gates:


And, nand, or, nor, xor, xnor, not, buf

WIRE: represents connections between elements.

How to use:

```
wire out1;           //declares there will be a connection named OUT1
and a1 (out1, input1, input2); //meaning:
                        //implement an AND gate
                        //named A1
                        //the output is OUT1
                        //the inputs are INPUT1, INPUT2
```


Building a multiplexer using gates

 

```
module e mux(input a, b, sel,
              output out, outbar);
  wire selb, out1, out2;
  not n1(selbar, sel);
  and a1(out1, a, sel);
  and a2(out2, b, selb);
  or o1(out, out1, out2);
  not n2(outbar, out)
endmodule e
```

The HDL

HDL = Hardware Description Language

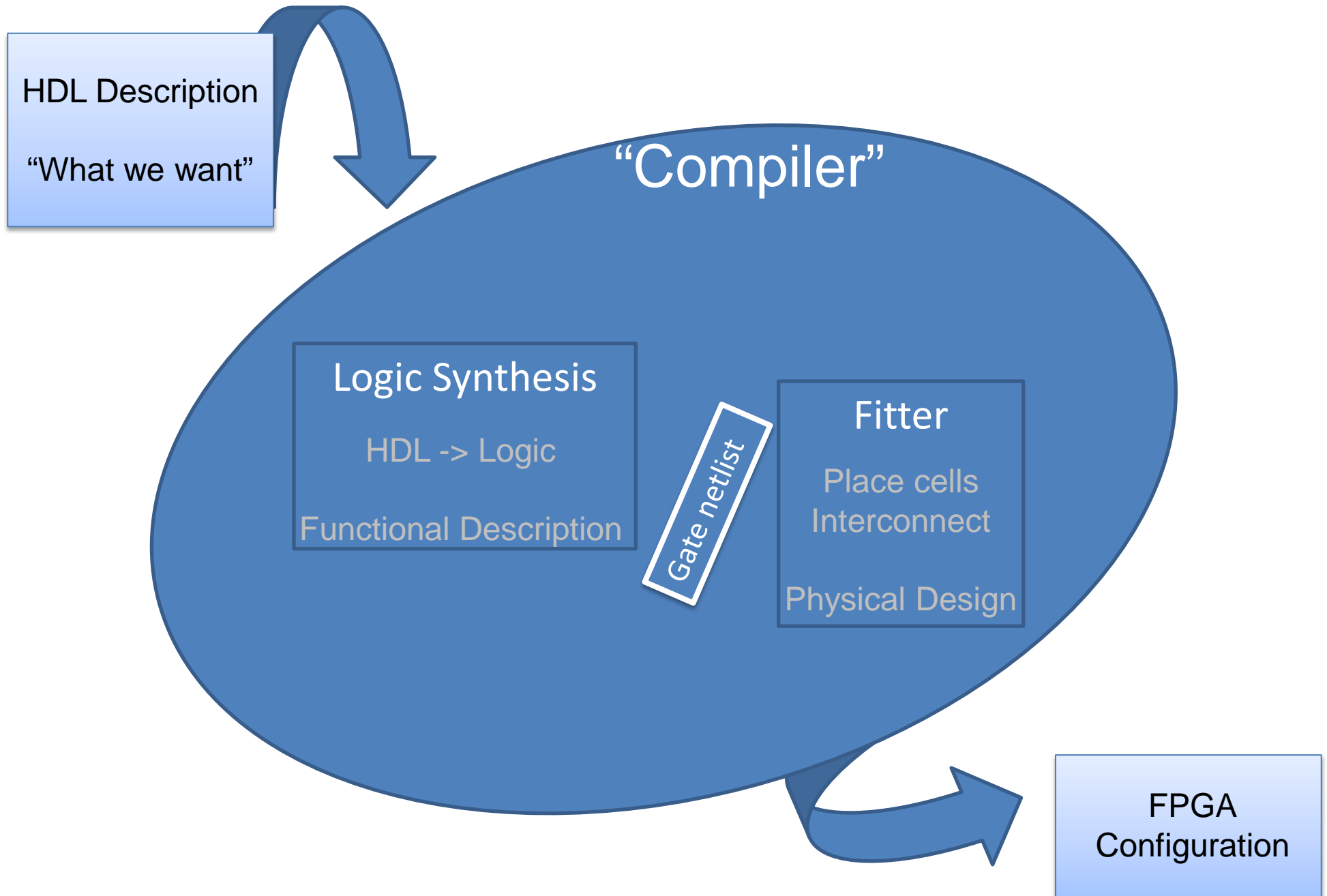

Verilog data values

Value	Meaning
0	Logic zero, “Low”
1	Logic one, “High”
Z or ?	High Impedance (tri-state)
X	Unknow (simulation)

Numeric constants

Full format: <Width>'<Radix>value

Width: number

Radix: d=decimal, h=hex, o=ocatl, b=binary

Value	Meaning
123	Default: decimal radix
'd123	'd=decimal radix
'h7B	'h=hexadecimal radix
'o173	'o=ocatl radix
'b111_101	'b=binary radix
16'b11111	A binary with 16 bits
16'd5	A 16 bit decimal = 'b0000_0000_0000_0101

Boolean operators

- **Bitwise operators** perform bit-oriented operations on vectors
 - $\sim(4'b0101) = \{\sim 0, \sim 1, \sim 0, \sim 1\} = 4'b1010$
 - $4'b0101 \& 4'b0011 = \{0\&0, 1\&0, 0\&1, 1\&1\} = 4'b0001$
- **Reduction operators** act on each bit of a single input vector
 - $\&(4'b0101) = 0 \& 1 \& 0 \& 1 = 1'b0$
- **Logical operators** return one-bit (true/false) results
 - $!(4'b0101) = 1'b0$

Bitwise

$\sim a$	NOT
$a \& b$	AND
$a b$	OR
$a \wedge b$	XOR
$a \sim\wedge b$ $a \wedge\sim b$	XNOR

Reduction

$\&a$	AND
$\sim\&a$	NAND
$ a$	OR
$\sim a$	NOR
$\wedge a$	XOR
$\sim\wedge a$ $\wedge\sim a$	XNOR

Logical

$!a$	NOT
$a \&\& b$	AND
$a b$	OR
$a == b$ $a != b$	[in]equality returns x when x or z in bits. Else returns 0 or 1
$a === b$ $a !== b$	case [in]equality returns 0 or 1 based on bit by bit comparison

*Note distinction between $\sim a$ and $!a$
when operating on multi-bit values*

Other operators

Conditional

$a ? b : c$	If a then b else c
-------------	--------------------

Relational

$a > b$	greater than
$a \geq b$	greater than or equal
$a < b$	Less than
$a \leq b$	Less than or equal

Arithmetic

$-a$	negate
$a + b$	add
$a - b$	subtract
$a * b$	multiply
a / b	divide
$a \% b$	modulus
$a ** b$	exponentiate
$a \ll b$	logical left shift
$a \gg b$	logical right shift
$a \lll b$	arithmetic left shift
$a \ggg b$	arithmetic right shift

How many bits?

Wire ab;	A 1 bit wire called <u>ab</u>
Wire ab,cd;	Two 1 bit wires called <u>ab</u> and <u>cd</u>
wire [31:0] ef;	A 32 bits wire bus called <u>ef</u> ;
{ab,cd}	Concatenation of <u>ab</u> and <u>cd</u> ;
ef[15]	Bit #15 (the sixteenth) of <u>ef</u>
ef[7:0]	First 8 bits of <u>ef</u> (the ones to the right)

What does this means?

wire [31:0] kk;
Wire [7:0] a,b,c,d;
Assign kk={d,c,b,a}

Note:

wire [7:0]a;

wire [0:7]b;

The two forms can be used. Prone to error if mixed.

Standard convention: [MSB:LSB] w/ MSB>LSB & LSB=0

[WIDTH-1:0]

The REG keyword

reg = register
is intended as a variable type

LeftHandSide inside always blocks must be reg!

For historical reasons...

reg is not always a clocked register (although it would make more sense)

reg can be used directly in the port declaration:

```
output reg [15:0] result
```

or in the declaration of a net:

```
reg a;  
reg[31:0] b;
```

Do not use reg with assigns:

```
reg out;  
assign out=0;
```

Continuous Assignments

(aka dataflow)

The assign construction
assign LHS = RHS ;
can use operators...

```
wire a, b, c, d, e, f, g;  
assign a=b;  
assign c=!d;  
assign e=f+g;
```

Sequential behaviours

(aka procedural)

The “always @” construction
always @ (sensitivity list)
begin
 LHS=RHS;
end
can use operators, if, case, ...

```
wire b, d, f, g;  
reg a, c, e;  
always @ (b, d, f, g)  
begin  
    a=b;  
    c=!d;  
    e=f+g;  
end
```

can be:
always @ (*)

The multiplexer using...

ASSIGN

```
// 2-to-1 multiplexer with dual-polarity outputs
module mux2(input a,b,sel, output z,zbar);
    // again order doesn't matter (concurrent execution!)
    // syntax is "assign LHS = RHS" where LHS is a wire/bus
    // and RHS is an expression
    assign z = sel ? b : a;
    assign zbar = ~z;
endmodule
```

ALWAYS @
IF...THEN...ELSE


```
// 4-to-1 multiplexer
module mux4(input a,b,c,d, input [1:0] sel, output reg z,zbar);
    always @(*) begin
        if (sel == 2'b00) z = a;
        else if (sel == 2'b01) z = b;
        else if (sel == 2'b10) z = c;
        else if (sel == 2'b11) z = d;
        else z = 1'bx; // when sel is X or Z
        // statement order matters inside always blocks
        // so the following assignment happens *after* the
        // if statement has been evaluated
        zbar = ~z;
    end
endmodule
```

ALWAYS @
CASE

```
// 4-to-1 multiplexer
module mux4(input a,b,c,d, input [1:0] sel, output reg z,zbar);
    always @(*) begin
        case (sel)
            2'b00: z = a;
            2'b01: z = b;
            2'b10: z = c;
            2'b11: z = d;
            default: z = 1'bx; // in case sel is X or Z
        endcase
        zbar = ~z;
    end
endmodule
```

Mix Assignments

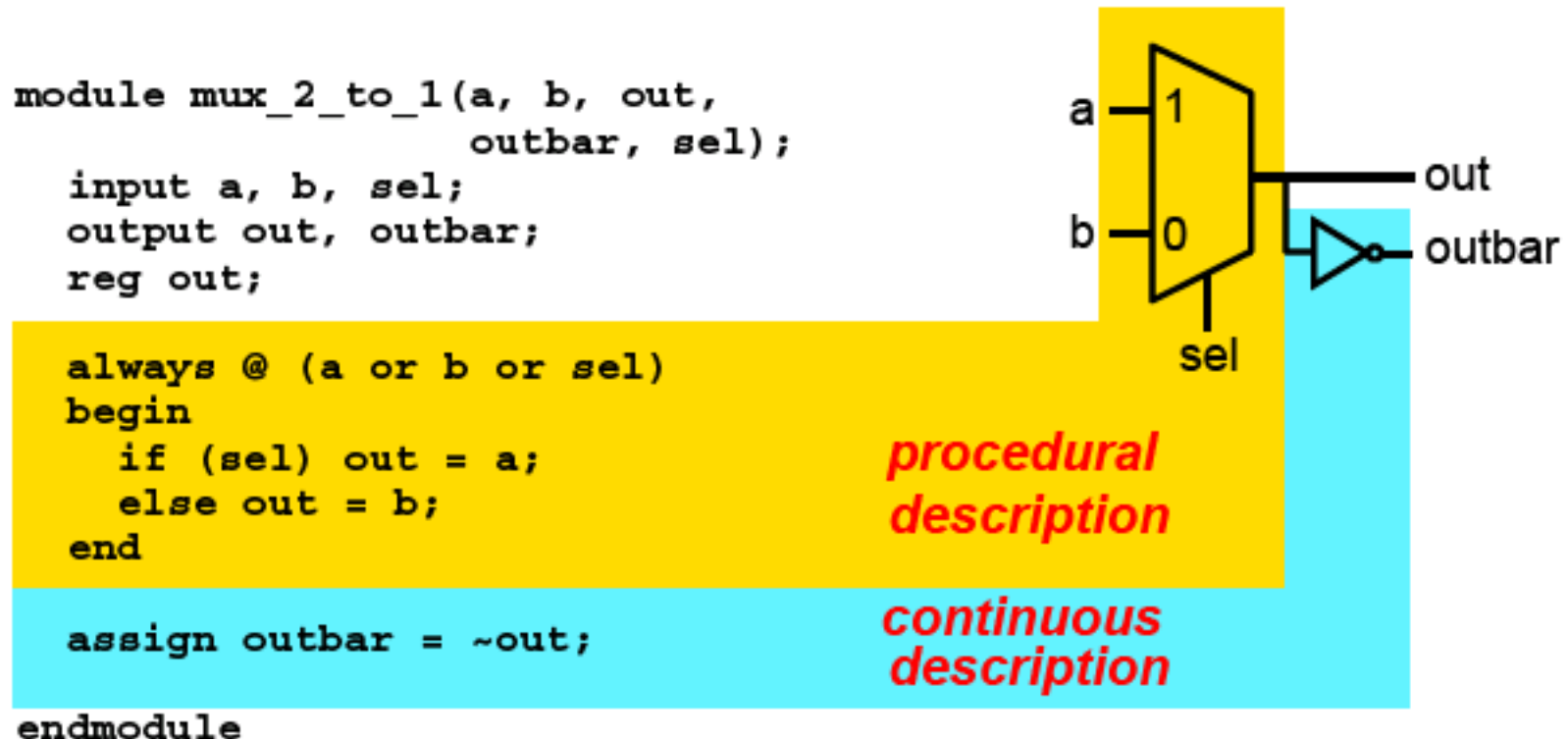
- Procedural and continuous assignments can (and often do) co-exist within a module
- Procedural assignments update the value of `reg`. The value will remain unchanged till another procedural assignment updates the variable. This is the main difference with continuous assignments in which the right hand expression is constantly placed on the left-side



n-bit signals

- Multi-bit signals and buses are easy in Verilog.
- 2-to-1 multiplexer with 8-bit operands:
 
```
module mux_2_to_1(a, b, out,  
                  outbar, sel);  
    input [7:0] a, b;  
    input sel;  
    output [7:0] out, outbar;  
    reg [7:0] out;  
    always @ (a or b or sel)  
    begin  
        if (sel) out = a;  
        else out = b;  
    end  
    assign outbar = ~out;  
endmodule
```



- {m,n} Concatenate m to n, creating larger vector

```
// if the MSB of a is high, this module  
// concatenates 1111 to the vector. With signed  
// binary numbers, this is called sign extension.
```

```
module sign_extend(a, out);  
    input [3:0] a;  
    output [7:0] out;  
  
    assign out = a[3] ? {4'b1111,a} : {4'b0000,a};  
endmodule
```

Integer Arithmetic

- Verilog's built-in arithmetic makes a 32-bit adder easy:


```
module add32(a, b, sum);  
    input[31:0] a,b;  
    output[31:0] sum;  
    assign sum = a + b;  
endmodule
```

- A 32-bit adder with carry-in and carry-out:

```
module add32_carry(a, b, cin, sum, cout);  
    input[31:0] a,b;  
    input cin;  
    output[31:0] sum;  
    output cout;  
    assign {cout, sum} = a + b + cin;  
endmodule
```

Danger

Goal:

 

Proposed Verilog Code:


```
module maybe_mux_3to1(a, b, c, sel, out)
    input [1:0] sel;
    input a,b,c;
    output out;
    reg out;

    always @(a or b or c or sel)
    begin
        case (sel)
            2'b00: out = a;
            2'b01: out = b;
            2'b10: out = c;
        endcase
    end
endmodule
```

If out is not assigned during any pass through the always block, then the **previous value must be retained**

LATCH

Synthesized Result:

 

- Latch memory “latches” old data when G=0 (we will discuss latches later)
- In practice, we almost *never* intend this

Solution:

- Precede all conditionals with a default assignment for all signals assigned within them...

```
always @(a or b or c or sel)
begin
    out = 1'bx;
    case (sel)
        2'b00: out = a;
        2'b01: out = b;
        2'b10: out = c;
    endcase
end
endmodule
```

```
always @(a or b or c or sel)
begin
    case (sel)
        2'b00: out = a;
        2'b01: out = b;
        2'b10: out = c;
        default: out = 1'bx;
    endcase
end
endmodule
```

- ...or, fully specify all branches of conditionals and assign all signals from all branches
 - For each if, include else
 - For each case, include default


Danger

Goal:

Proposed Verilog Code:

Code: if $i[0]$ is 1, the result is 00 regardless of the other inputs.
 $i[0]$ takes the highest priority.

4-to-2 Binary Encoder

 


I_3	I_2	I_1	I_0	E_1	E_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1
all others				X	X

```
module binary_encoder(i, e);
    input [3:0] i;
    output [1:0] e;
    reg [1:0] e;

    always @(i)
    begin
        if (i[0]) e = 2'b00;
        else if (i[1]) e = 2'b01;
        else if (i[2]) e = 2'b10;
        else if (i[3]) e = 2'b11;
        else e = 2'bxx;
    end
endmodule
```

```
if (i[0]) e = 2'b00;
else if (i[1]) e = 2'b01;
else if (i[2]) e = 2'b10;
else if (i[3]) e = 2'b11;
else e = 2'bxx;
end
```

Inferred Result:

 

What is the resulting circuit?

If-else and case statements are interpreted very literally!
Beware of unintended priority logic

Solution:


- Make sure that if-else and case statements are *parallel*
 - If **mutually exclusive conditions** are chosen for each branch...
 - ...then synthesis tool can generate a simpler circuit that evaluates the branches in parallel

Parallel Code:

```
module binary_encoder(i, e);
    input [3:0] i;
    output [1:0] e;
    reg [1:0] e;

    always @(i)
    begin
        if (i == 4'b0001) e = 2'b00;
        else if (i == 4'b0010) e = 2'b01;
        else if (i == 4'b0100) e = 2'b10;
        else if (i == 4'b1000) e = 2'b11;
        else e = 2'bxx;
    end
endmodule
```

Minimized Result:

 


Modules,
again, and
again and
again...

Structuring... Modules

Modules are the building blocks in Verilog!

 There is at least one module: The top one that has the name of the project!



Ports in the top level module link directly to the pins

Modules with different juice...

```
module mux(input a, b, sel, output q, qbar);
```

```
wire selbar, q1, q2;  
not n1(selbar, sel);  
and a1(q1, a, selbar);  
and a2(q2, b, sel);  
or o1(q, q1, q2);  
not n2(qbar, q)
```

```
assign q = sel ? a : b;  
assign qbar = ~ q;
```

```
always @ (a, b, sel)  
begin  
  if (sel) q=a;  
  else q=b;  
end  
assign qbar = ~ q;
```

```
endmodule
```

We just need to know the shell, the interface, and its function!

Call the port by its name!

```
module mux(i0, i1, i2, sel, out);
```


Option 1: Know the order and write all ports...

```
mux my_mux (add_out, sub_out, mul_out, f[1:0], res);
```

Option 2: Know their names...

syntax: `module_type module_name (.port_name(net_name), .port2_name(net2_name));`
 
```
mux my_mux (. i0(add_out),  
              . i1(sub_out),  
              . i2(mul_out),  
              . sel(f[1:0]),  
              . out(res));
```



OR

```
mux my_mux (. sel(f[1:0]),  
              . out(res),  
              . i0(add_out),  
              . i1(sub_out),  
              . i2(mul_out),  
              );
```

OR
even

```
mux my_mux (. sel(2'b00),  
              . out(res),  
              . i0(add_out),  
              );
```

Parametrized modules

could be useful if we could build “generic” modules
for instance a mux for data buses that can be 1 bit to 32bit
if we have a parameter that seems easy

THE #(PARAMETER)

```
module mux #(parameter W=1)
    (input [W-1:0] i0, i1)
    output [W-1] out
    input sel);
    assign out = sel ? i1 : i0;
endmodule
```

parameter named “W”
default=1

Using a parametrized module

```
wire a, b, c, z;
mux #(. W(1)) m1(. sel(a), . i0(b), . i1(c), . out(z));
```

```
wire aa;
wire [15:0] bb, cc, zz;
mux #(. W(16)) m1(. sel(aa), . i0(bb), . i1(cc), . out(zz));
```

and of course... be creative...

You can instantiate lots of modules that feeds one another...
Each instance is like a “new chip” of that type
Each instance must have different names

How many instances can drive a net??


Sometimes drawing in a paper is useful...
just draw boxes, don't need to be an artist...

```
// 4-to-1 multiplexer
module mux4(input d0,d1,d2,d3, input [1:0] sel, output z);
  wire z1,z2;
  // instances must have unique names within current module.
  // connections are made using .portname(expression) syntax.
  // once again order doesn't matter...
  mux2 m1(.sel(sel[0]),.a(d0),.b(d1),.z(z1)); // not using zbar
  mux2 m2(.sel(sel[0]),.a(d2),.b(d3),.z(z2));
  mux2 m3(.sel(sel[1]),.a(z1),.b(z2),.z(z));
  // could also write "mux2 m3(z1,z2,sel[1],z,)" NOT A GOOD IDEA!
endmodule
```

Build an ALU

Connecting modules to build complex machines

Example: A 32-bit ALU

 

Function Table

F2	F1	F0	Function
0	0	0	$A + B$
0	0	1	$A + 1$
0	1	0	$A - B$
0	1	1	$A - 1$
1	0	X	$A * B$

Modules

2-to-1 MUX

```
module mux32two(i0,i1,sel,out);
input [31:0] i0,i1;
input sel;
output [31:0] out;

assign out = sel ? i1 : i0;

endmodule
```

3-to-1 MUX

```
module mux32three(i0,i1,i2,sel,out);
input [31:0] i0,i1,i2;
input [1:0] sel;
output [31:0] out;
reg [31:0] out;

always @ (i0 or i1 or i2 or sel)
begin
    case (sel)
        2'b00: out = i0;
        2'b01: out = i1;
        2'b10: out = i2;
        default: out = 32'bx;
    endcase
end
endmodule
```

32-bit Adder

```
module add32(i0,i1,sum);
input [31:0] i0,i1;
output [31:0] sum;

assign sum = i0 + i1;

endmodule
```

32-bit Subtractor

```
module sub32(i0,i1,diff);
input [31:0] i0,i1;
output [31:0] diff;

assign diff = i0 - i1;

endmodule
```

16-bit Multiplier

```
module mul16(i0,i1,prod);
input [15:0] i0,i1;
output [31:0] prod;

// this is a magnitude multiplier
// signed arithmetic later
assign prod = i0 * i1;

endmodule
```

Top-Level: connect the modules

■ Given submodules:

```
module mux32two(i0,i1,sel,out);  
module mux32three(i0,i1,i2,sel,out);  
module add32(i0,i1,sum);  
module sub32(i0,i1,diff);  
module mul16(i0,i1,prod);
```

■ Declaration of the ALU Module:

```
module alu(a, b, f, r);  
  input [31:0] a, b;  
  input [2:0] f;  
  output [31:0] r;
```

```
  wire [31:0] addmux_out, submux_out;  
  wire [31:0] add_out, sub_out, mul_out;
```


```
  mux32two    adder_mux(b, 32'd1, f[0], addmux_out);  
  mux32two    sub_mux(b, 32'd1, f[0], submux_out);  
  add32       our_adder(a, addmux_out, add_out);  
  sub32       our_subtractor(a, submux_out, sub_out);  
  mul16       our_multiplier(a[15:0], b[15:0], mul_out);  
  mux32three  output_mux(add_out, sub_out, mul_out, f[2:1], r);
```

endmodule

module
names

(unique)
instance
names

corresponding
wires/regs in
module alu

 


intermediate output nodes ●

Until here: Combinational logic

Sequential Logic

Something We Can't Build (Yet)

 What if you were given the following design specification:




What makes this circuit so different from those we've discussed before?

1. "State" - i.e. the circuit has memory
2. The output was changed by a input "event" (pushing a button) rather than an input "value"

Digital State

One model of what we'd like to build

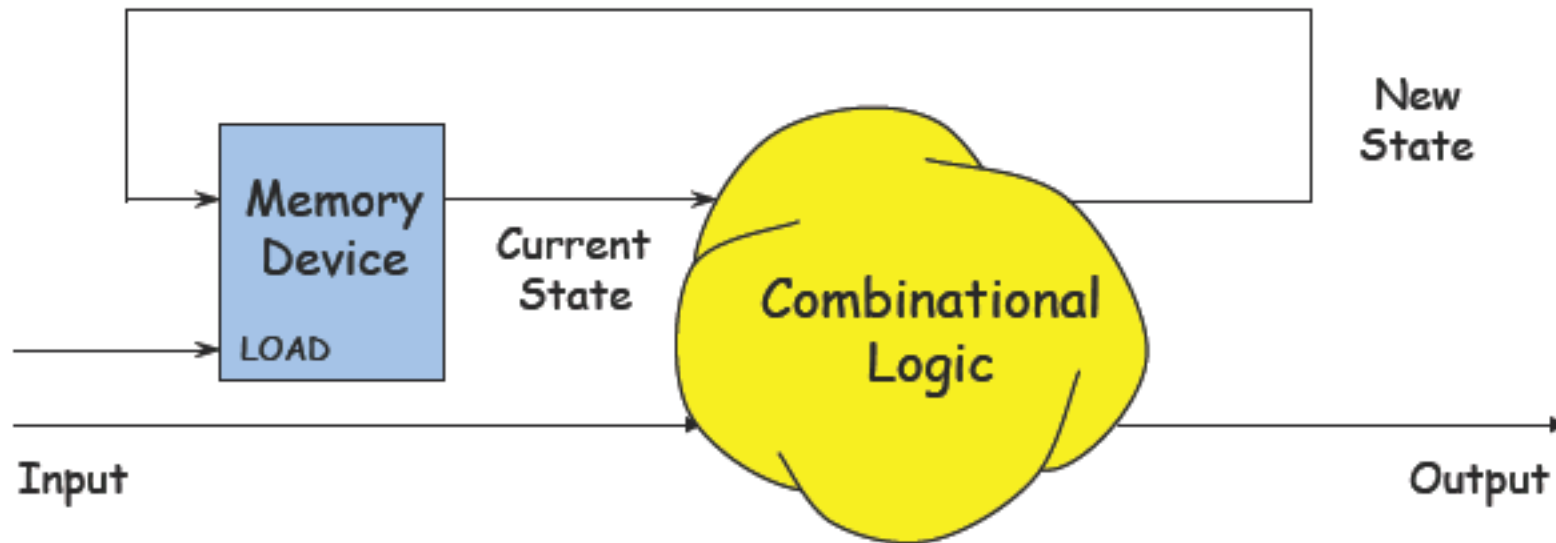



Plan: Build a Sequential Circuit with stored digital STATE -

- Memory stores CURRENT state, produced at output
- Combinational Logic computes
 - NEXT state (from input, current state)
 - OUTPUT bit (from input, current state)
- State changes on LOAD control input

When Output depends on input and current state, circuit is called a Mealy machine. If Output depends only on the current state, circuit is called a Moore machine.

Our next building block: the D register

  The edge-triggered D register: *on the rising edge of CLK*, the value of D is saved in the register and then shortly afterwards appears on Q.




The Sequential **always** Block

Edge-triggered circuits are described using a sequential **always** block


Combinational
 
```
module comb(input a, b, sel,
            output reg out);
  always @(*) begin
    if (sel) out = a;
    else out = b;
  end
endmodule
```



Sequential
 
```
module seq(input a, b, sel, clk,
            output reg out);
  always @(posedge clk) begin
    if (sel) out <= a;
    else out <= b;
  end
endmodule
```



Importance of the Sensitivity List

- The use of `posedge` and `negedge` makes an `always` block sequential (edge-triggered)
- Unlike a combinational `always` block, the sensitivity list **does** determine behavior for synthesis!

*D-Register with **synchronous** clear*

```
module dff_sync_clear(  
    input d, clearb, clock,  
    output reg q  
);  
    always @(posedge clock)  
    begin  
        if (!clearb) q <= 1'b0;  
        else q <= d;  
    end  
endmodule
```

`always` block entered only at each positive clock edge

*D-Register with **asynchronous** clear*

```
module dff_sync_clear(  
    input d, clearb, clock,  
    output reg q  
);  
    always @(negedge clearb or posedge clock)  
    begin  
        if (!clearb) q <= 1'b0;  
        else q <= d;  
    end  
endmodule
```

`always` block entered immediately when (active-low) `clearb` is asserted

Note: The following is incorrect syntax: `always @(clear or negedge clock)`
If one signal in the sensitivity list uses `posedge/negedge`, then all signals must.

- Assign any signal or variable from only one `always` block. Be wary of race conditions: `always` blocks with same trigger execute concurrently...

Blocking vs. Nonblocking Assignments

- Verilog supports two types of assignments within `always` blocks, with subtly different behaviors.
- *Blocking assignment* (`=`): evaluation and assignment are immediate

```
always @(*) begin
  x = a | b;      // 1. evaluate a|b, assign result to x
  y = a ^ b ^ c;  // 2. evaluate a^b^c, assign result to y
  z = b & ~c;     // 3. evaluate b&(~c), assign result to z
end
```


Nonblocking assignment (`<=`): all assignments deferred to end of simulation time step after all right-hand sides have been evaluated (even those in other active `always` blocks)

```
always @(*) begin
  x <= a | b;      // 1. evaluate a|b, but defer assignment to x
  y <= a ^ b ^ c;  // 2. evaluate a^b^c, but defer assignment to y
  z <= b & ~c;     // 3. evaluate b&(~c), but defer assignment to z
  // 4. end of time step: assign new values to x, y and z
end
```

Sometimes, as above, both produce the same result. Sometimes, not!

Assignment styles for sequential logic

Flip-Flop Based Digital Delay Line

 

- Will nonblocking and blocking assignments both produce the desired result?


```
module nonblocking(in, clk, out);  
  input in, clk;  
  output out;  
  reg q1, q2, out;  
  always @ (posedge clk)  
  begin  
    q1 <= in;  
    q2 <= q1;  
    out <= q2;  
  end  
endmodule
```

```
module blocking(in, clk, out);  
  input in, clk;  
  output out;  
  reg q1, q2, out;  
  always @ (posedge clk)  
  begin  
    q1 = in;  
    q2 = q1;  
    out = q2;  
  end  
endmodule
```

Use nonblocking for sequential logic

```
always @ (posedge clk)
begin
    q1 <= in;
    q2 <= q1;
    out <= q2;
end
```

 “At each rising clock edge, $q1$, $q2$, and out **simultaneously receive the old values** of in , $q1$, and $q2$.”




```
always @ (posedge clk)
begin
    q1 = in;
    q2 = q1;
    out = q2;
end
```

“At each rising clock edge, $q1 = in$.

After that, $q2 = q1 = in$.

After that, $out = q2 = q1 = in$.

Therefore $out = in$.”

 


- Blocking assignments do not reflect the intrinsic behavior of multi-stage sequential logic
- **Guideline: use nonblocking assignments for sequential always blocks**

Use blocking for combinational logic

Blocking Behavior

	a	b	c	x	y
(Given) Initial Condition	1	1	0	1	1
a changes; always block triggered	0	1	0	1	1
x = a & b;	0	1	0	0	1
y = x c;	0	1	0	0	0

 

```

module blocking(a,b,c,x,y);
  input a,b,c;
  output x,y;
  reg x,y;

  always @ (a or b or c)
  begin
    x = a & b;
    y = x | c;
  end
endmodule
  
```

Nonblocking Behavior

	a	b	c	x	y	Deferred
(Given) Initial Condition	1	1	0	1	1	
a changes; always block triggered	0	1	0	1	1	
x <= a & b;	0	1	0	1	1	x<=0
y <= x c;	0	1	0	1	1	x<=0, y<=1
Assignment completion	0	1	0	0	1	

```

module nonblocking(a,b,c,x,y);
  input a,b,c;
  output x,y;
  reg x,y;

  always @ (a or b or c)
  begin
    x <= a & b;
    y <= x | c;
  end
endmodule
  
```

- Nonblocking and blocking assignments will synthesize correctly. Will both styles simulate correctly?
- Nonblocking assignments do not reflect the intrinsic behavior of multi-stage combinational logic
- While nonblocking assignments can be hacked to simulate correctly (expand the sensitivity list), it's not elegant
- **Guideline: use blocking assignments for combinational always blocks**


= vs <= inside always

```
always @(posedge clk) begin
    a = b;    // blocking assignment
    b = a;    // execute sequentially
end
```

```
always @(posedge clk) begin
    a <= b;   // non-blocking assignment
    b <= a;   // eval all RHSs first
end
```

Rule: always change state using <= (e.g., inside always @(posedge clk)...)

Example: A simple counter

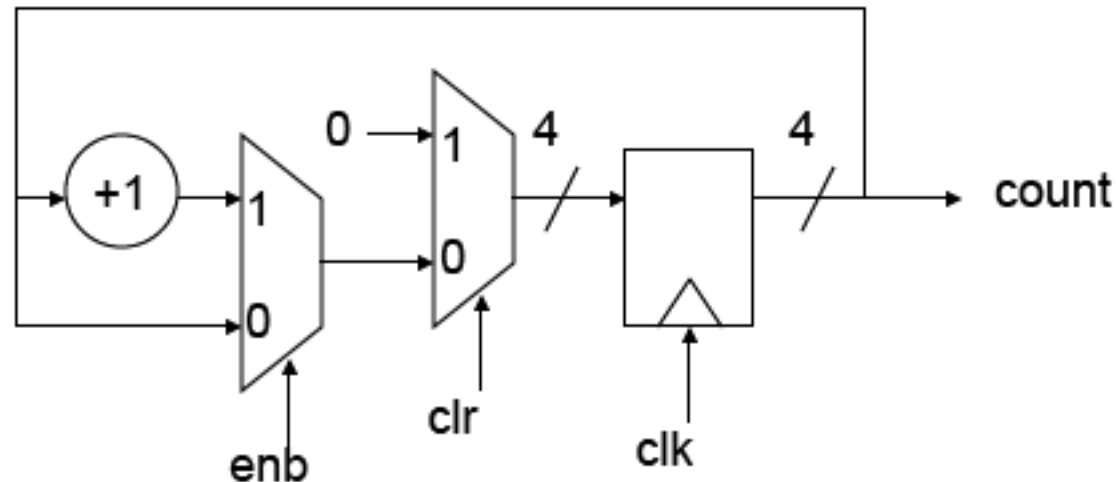

```
// 4-bit counter with enable and synchronous clear
module counter(input clk,enb,clr,
               output reg [3:0] count);
    always @(posedge clk) begin
        count <= clr ? 4'b0 : (enb ? count+1 : count);
    end
endmodule
```

Counter 32 bits in the leds...

```
reg [31:0] count ;

assign LEDR = count[17:0];
always @ (posedge CLOCK_50)
begin
    count <= count +1;
end
```

PWM – Pulse Width Modulation



```
wire [7:0] H_PWM;
wire [3:0] bright;
assign bright=SW[3:0];
reg [3:0] PWM_count;
always @ (posedge CLOCK_50)
    PWM_count<=PWM_count+1;
assign H_PWM=(bright>PWM_count)? 7'hFF : 7'h00;
```


The Asynchronous counter

A simple counter architecture

- uses only registers
(e.g., 74HC393 uses T-register and negative edge-clocking)
- Toggle rate fastest for the LSB

 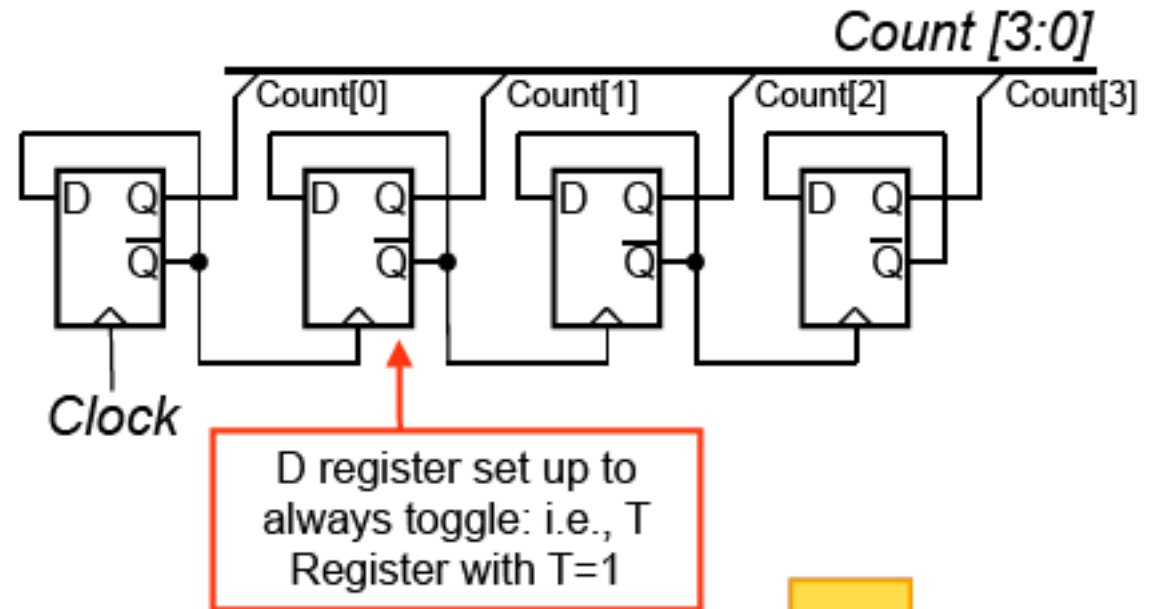...but ripple architecture leads to large skew between outputs




The ripple counter in verilog

Single D Register with Asynchronous Clear:

```
module dreg_async_reset (clk, clear, d, q, qbar);
input d, clk, clear;
output q, qbar;
reg q;

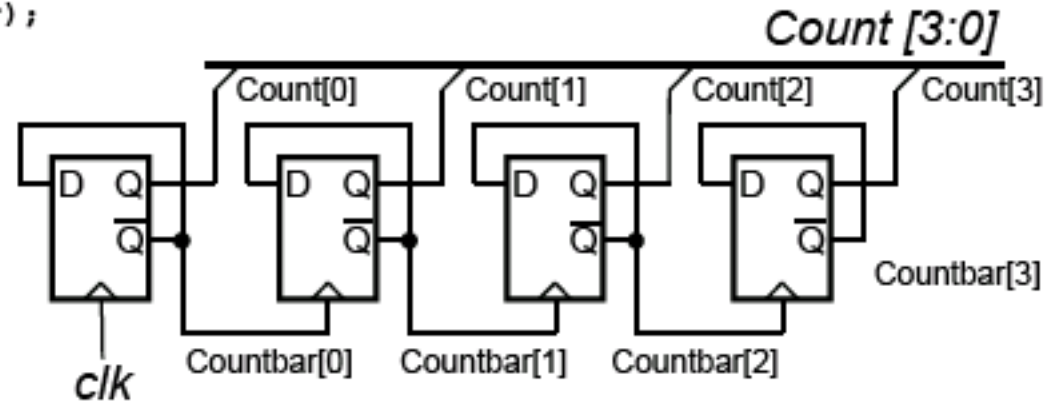always @ (posedge clk or negedge clear)
begin
if (!clear)
q <= 1'b0;
else q <= d;
end
assign qbar = ~q;
endmodule
```



Structural Description of Four-bit Ripple Counter:


```
module ripple_counter (clk, count, clear);
input clk, clear;
output [3:0] count;
wire [3:0] count, countbar;

dreg_async_reset bit0(.clk(clk), .clear(clear), .d(countbar[0]),
    .q(count[0]), .qbar(countbar[0]));
dreg_async_reset bit1(.clk(countbar[0]), .clear(clear), .d(countbar[1]),
    .q(count[1]), .qbar(countbar[1]));
dreg_async_reset bit2(.clk(countbar[1]), .clear(clear), .d(countbar[2]),
    .q(count[2]), .qbar(countbar[2]));
dreg_async_reset bit3(.clk(countbar[2]), .clear(clear), .d(countbar[3]),
    .q(count[3]), .qbar(countbar[3]));


endmodule
```

Logic for a synchronous counter

- Count (C) will be retained by a D Register
- Next value of counter (N) computed by combinational logic
- Any time multiple bits change, the counter output needs time to settle.
- Even though all flip-flops share the same clock, individual bits will change at different times.
 - Clock skew, propagation time variations
- Can cause glitches in combinational logic driven by the counter
- The RCO can also have a glitch.

 

 **Care is required of the
Ripple Carry Output:
It can have glitches:
Any of these transition
paths are possible!**



TOOLS

Tools - Simulation

Verilog


Example: Mux




System Tasks & Functions

Quartus II support for **system tasks** and functions is described below. See *Description Language Based on the Verilog Hardware Description Language*

Section	Verilog HDL Construct	Quartus II Support <u>(1)</u>	<u>Note</u>
14.1	Display System Tasks	Not supported.	
14.2	File Input-Output System Tasks	Not supported.	
14.3	Timescale System Tasks	Not supported.	
14.4	Simulation Control System Tasks	Not supported.	
14.5	Timing Check System Tasks	Not supported.	
14.6	PLA Modeling System Tasks	Not supported.	
14.7	Stochastic Analysis System Tasks	Not supported.	
14.8	Simulation Time System Functions	Not supported.	
14.9	Conversion Functions for Reals	Not supported.	
14.10	Probabilistic Distribution Functions	Not supported.	

 

Quartus II

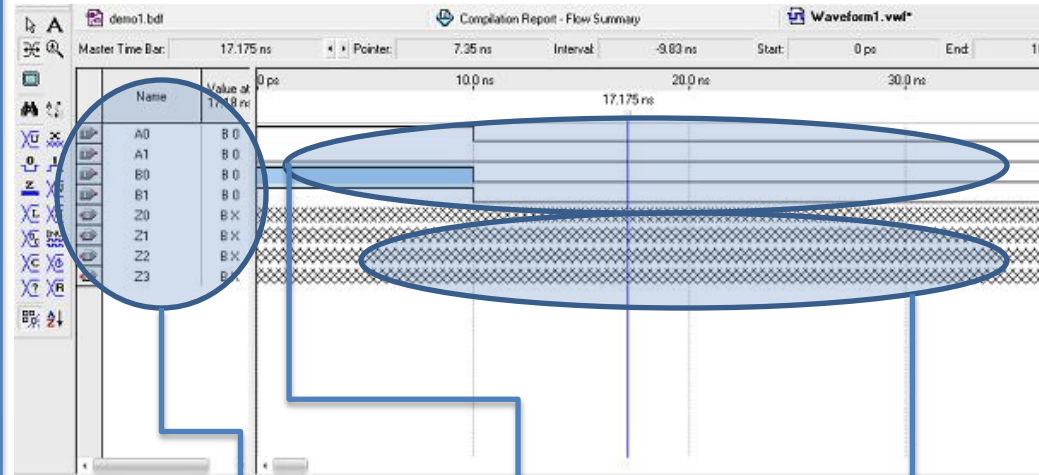



Define the signals :
Inputs – stimulus
Outputs - results

Define the stimulus to the system


Run the simulation and you get the result

Tools – Measurement instruments

Waveforms

  


Logic Levels

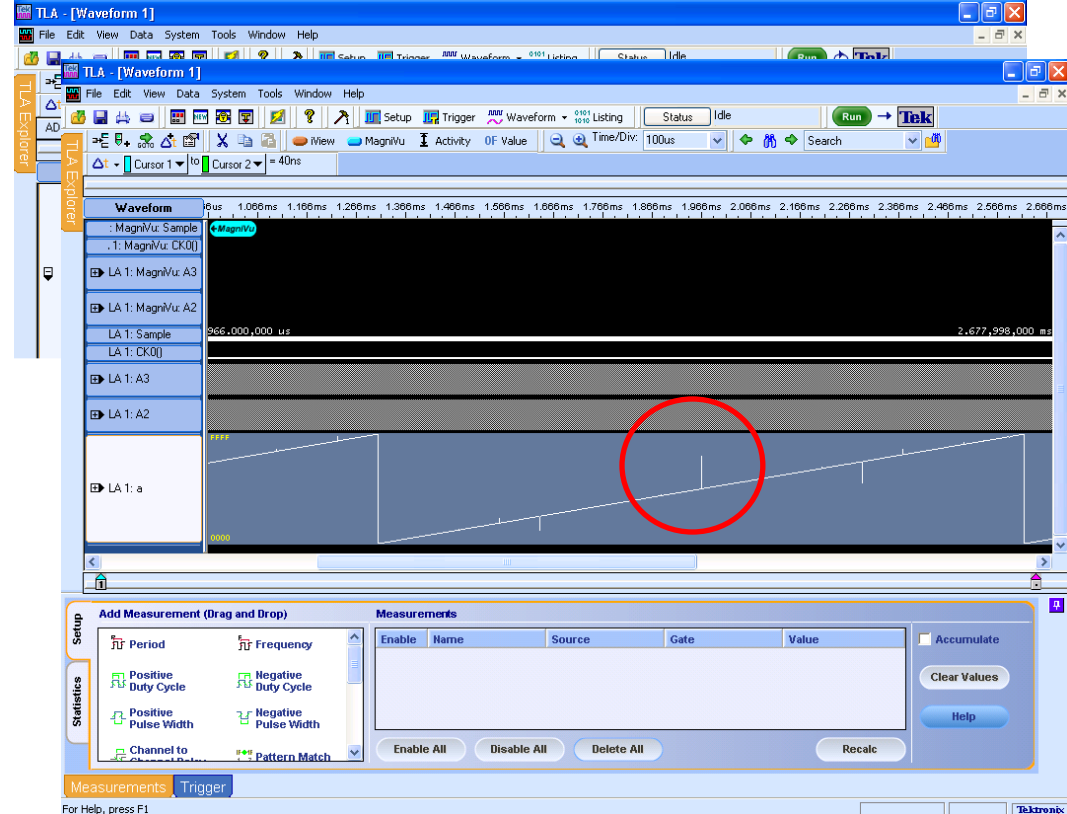

Tools – Internal Logic Analyser

Signal-TAP embedded Logic Analyser

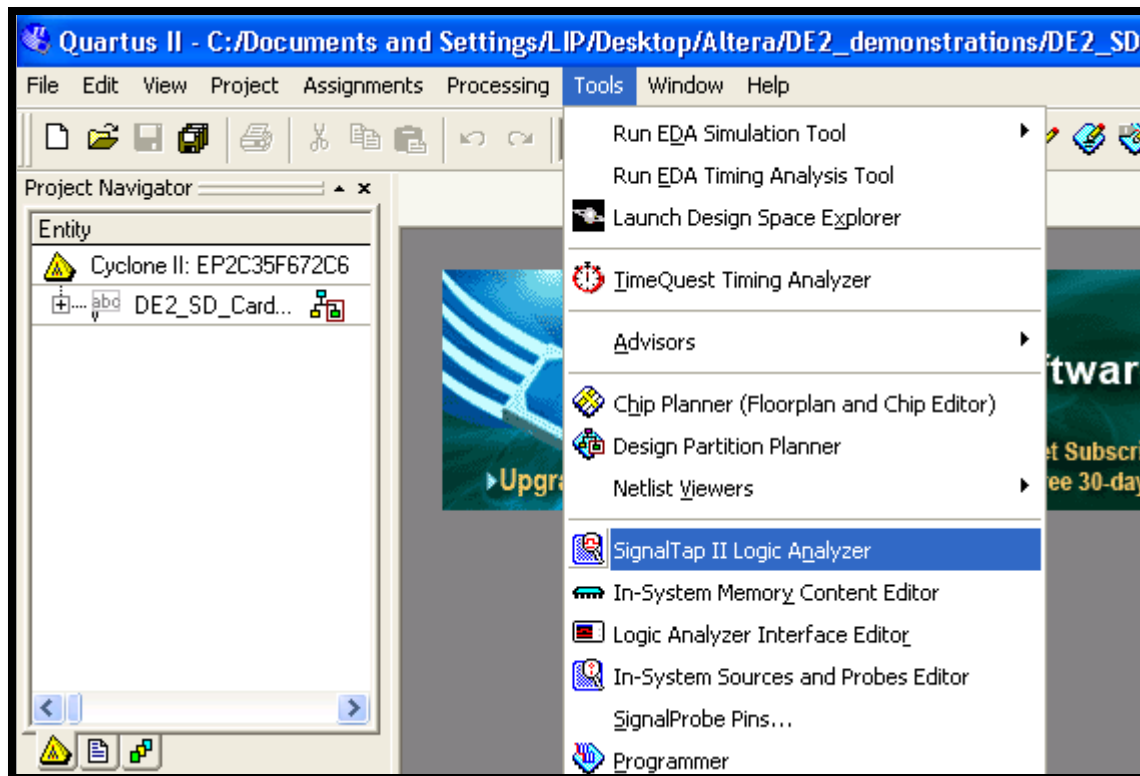Quartus II Handbook Version 9.0 Volume 3: Verification
14. Design Debugging Using the
SignalTap II Embedded Logic Analyzer



Tools – Internal Logic Analyser

The screenshot shows the Quartus II Internal Logic Analyser interface. The main window is titled "Quartus II - C:/Documents and Settings/LIP/Desktop/Altera/DE2_SD_Card_Audio/DE2_SD_Card_Audio - DE2_SD_Card_Audio - [stp1.stp]". The interface includes a menu bar (File, Edit, View, Project, Processing, Tools, Window), a toolbar, and several panels. The "Instance Manager" panel at the top left shows a table with columns: Instance, Status, LEs, Memory, M512_MLAB, M4K_M9K, and M-RAM. The "JTAG Chain Configuration" panel at the top right shows "No device is selected". The "Signal Configuration" panel on the right is divided into "Clock" and "Data" sections. The "Data" section includes "Sample depth" (128), "RAM type" (Auto), "Segmented" (2 64 sample segments), "Storage qualifier" (Type: Continuous), and "Input port". The "Trigger" section includes "Trigger flow control" (Sequential), "Trigger position" (Pre trigger position), and "Trigger conditions" (1). The "Hierarchy Display" panel at the bottom left shows a tree view with "auto_singaltap_0". The "Data Log" panel at the bottom right shows a table with columns: Type, Alias, Name, Data Enable, Trigger Enable, and Trigger Conditions. The "Data" tab is selected, showing a table with columns: Type, Alias, Name, Data Enable, Trigger Enable, and Trigger Conditions. The "Setup" tab is also visible. Red arrows point from the text labels on the right to the corresponding panels in the interface.

Invalid JTAG configuration

Instance Manager:

Instance	Status	LEs	Memory	M512_MLAB	M4K_M9K	M-RAM
auto_singaltap_0	Not running	0 cells	0 bits	NA	NA	NA

JTAG Chain Configuration: No device is selected

Hardware: Disabled

Device: None Detected

SDF Manager:

auto_singaltap_0

Type	Alias	Name	Data Enable	Trigger Enable	Trigger Conditions
			0	0	1 Basic

Signal Configuration:

Clock:

Data

Sample depth: 128 RAM type: Auto

Segmented: 2 64 sample segments

Storage qualifier

Type: Continuous

Input port:

Record data discontinuities

Disable storage qualifier

Trigger

Trigger flow control: Sequential

Trigger position: Pre trigger position

Trigger conditions: 1

Hierarchy Display:

Data Log:

auto_singaltap_0

auto_singaltap_0

For Help, press F1

CONTROL


Clock
definition

Trigger
definition

The signal
you want to
"see"

Tools – Internal Logic Analyser

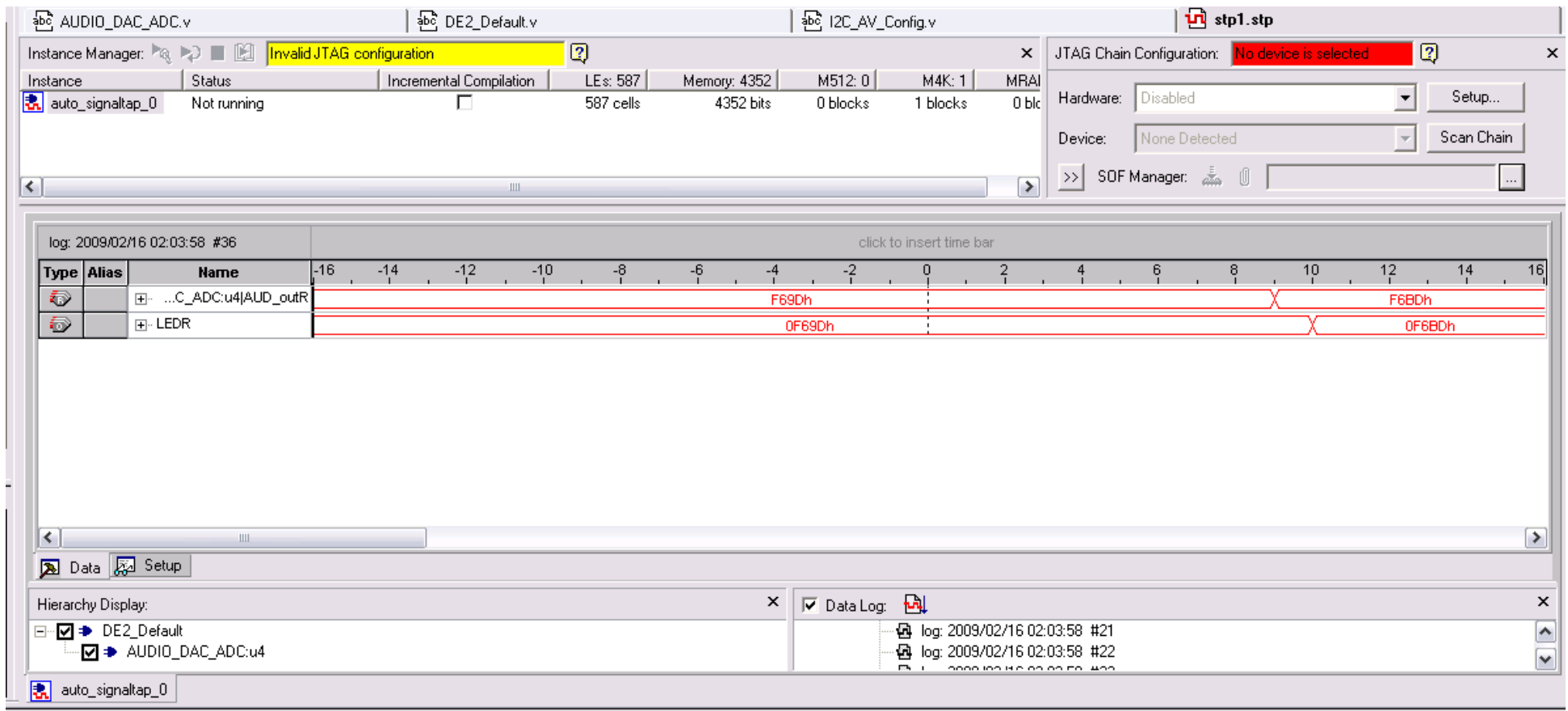The logic analyser will collect data from the registers and output it through the JTAG programming interface



Tools – Signal probe

Internal signals can be extracted to output pins and connected to an external logic analyser. Signals can be exchanged easily...

SignalTap step by step

- Open DE2 default and compile it!
- Program DE2
- Tools→Signal TapII Logic Analyser

The screenshot shows the Quartus II SignalTap II Logic Analyzer interface. The top status bar indicates an "Invalid JTAG configuration" error. The Instance Manager shows the "auto_sigtap_0" instance is "Not running". The Signal Configuration dialog is open, showing the "JTAG Chain Configuration" tab with a red error message "No device is selected". The "Signal Configuration" tab is also visible, showing settings for the signal tap.

Invalid JTAG configuration

Instance Manager:

Instance	Status	LEs: 0	Memory: 0	M512,MLAB: 0/0	M4K,M9K: 75/105	M-RAM,M144K: 0/0
auto_sigtap_0	Not running	0 cells	0 bits	NA	NA	NA

JTAG Chain Configuration: No device is selected

Hardware: Please Select **Setup...**

Device: None Detected **Scan Chain**

>> SOF Manager:

Signal Configuration:

Clock:

Data

Sample depth: 128 RAM type: Auto

☐ Segmented: 2 64 sample segments

Storage qualifier

Type: Continuous

Input port:

☐ Record data discontinuities

☐ Disable storage qualifier

Trigger

Trigger flow control: Sequential

auto_sigtap_0 Allow all changes

Node		Data Enable	Trigger Enable	Trigger Conditions	
Type	Alias	Name	0	0	1 <input checked="" type="checkbox"/> Basic
Double-click to add nodes					


Hierarchy Display:

Data Log:


- auto_sigtap_0

For Help, press F1

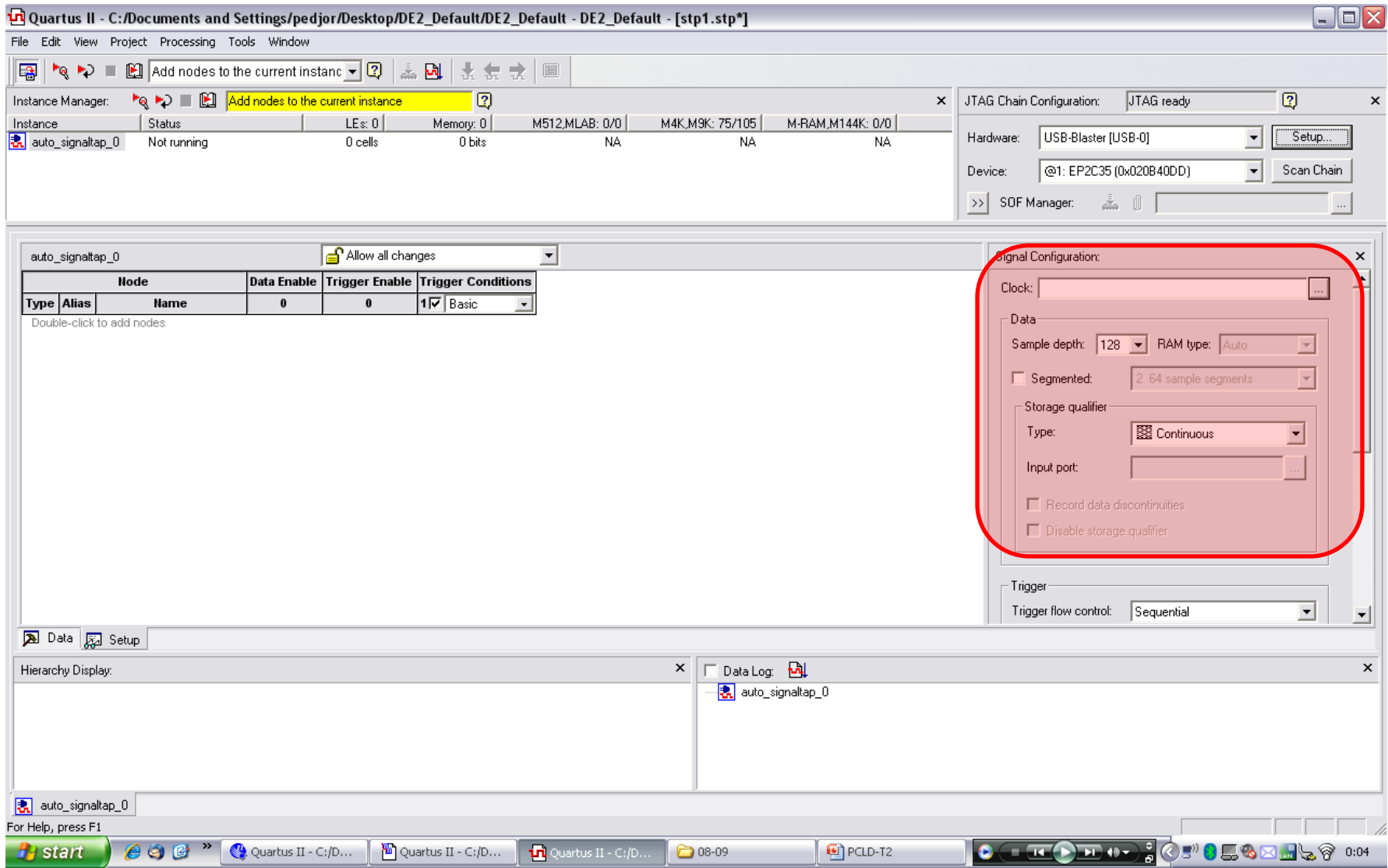
- Setup the hardware (choose the USB blaster)



- Define the clock


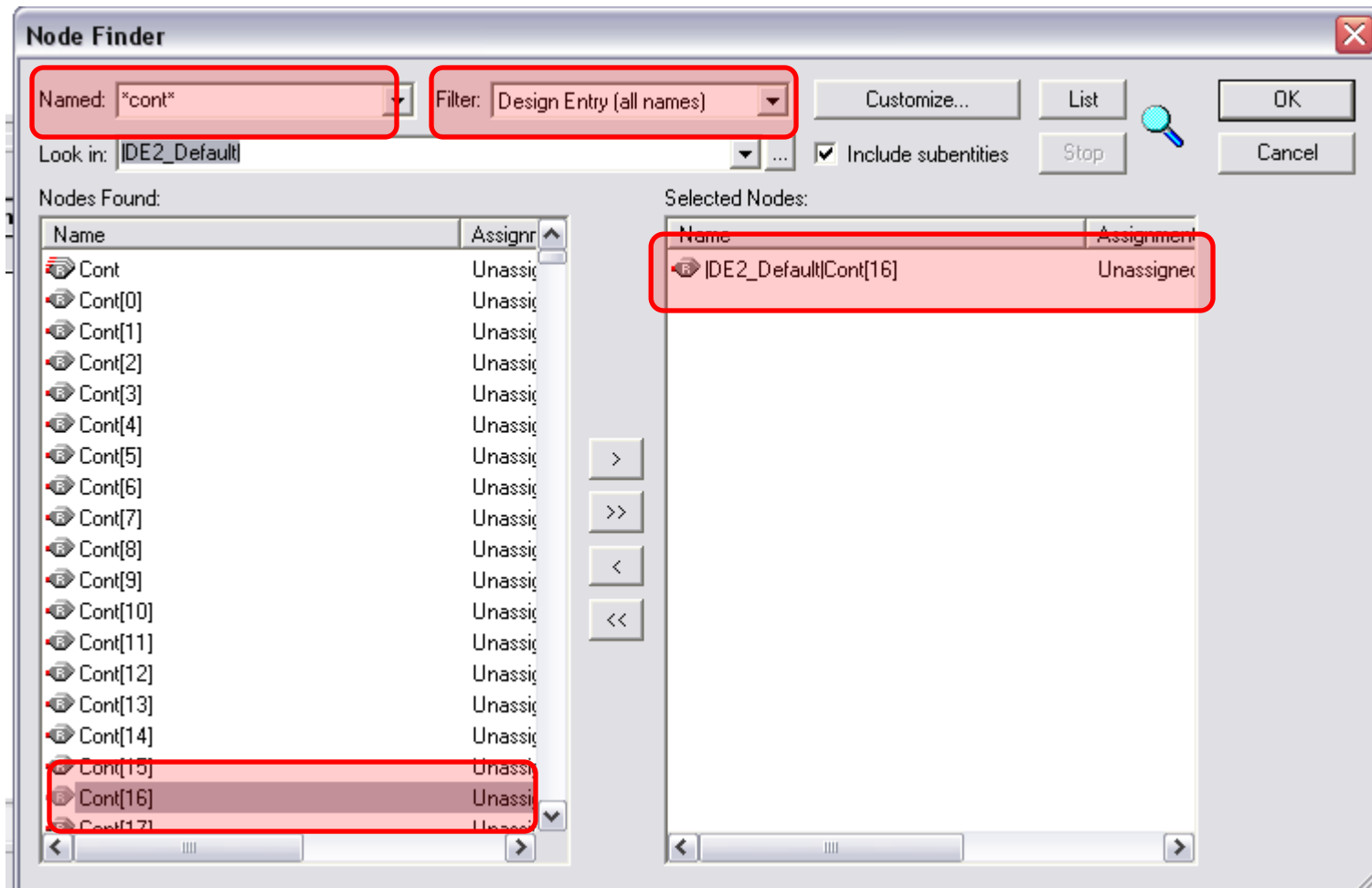


 Choose the signals to observe. Choose Cont 25,24,23,22



- Compile the project! You may need to save some files and answer some questions
- Program the board

  Run Analysis → Green (acquisition in progress, acquiring data)





Run Analysis (1 time)


Run Analysis (continuous)

Stop


Finally: data!!

 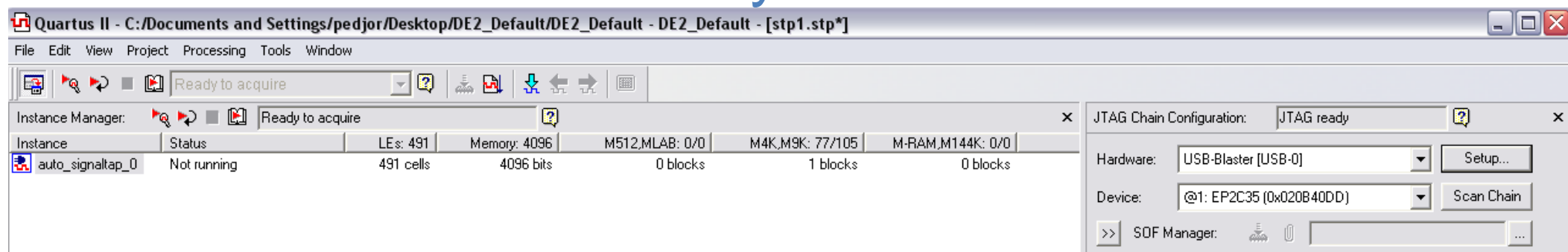


- Select the four signals;
- Edit→group

 

 - Select the group
- Edit→Bus Display Format→Unsigned Line Chart




- Unzoom

 




Implementation for on/off button

 
 
```
module onoff(input button, output reg light);  
    always @(posedge button) light <= ~light;  
endmodule
```



Synchronous on/off button

When designing a system that accepts many inputs it would be hard to have input changes serve as the system clock (which input would we use?). So we'll use a single clock of some fixed frequency and have the inputs control what state changes happen on rising clock edges.

```
module onoff_sync(input clk, button,
                  output reg light);
    always @ (posedge clk) begin
        if (button) light <= ~light;
    end
endmodule
```



Resetting to a known state

Usually one can't rely on registers powering-on to a particular initial state*. So most designs have a RESET signal that when asserted initializes all the state to known, mutually consistent initial values.

```
module onoff_sync(input clk, reset, button,
                  output reg light);
    always @ (posedge clk) begin
        if (reset) light <= 0;
        else if (button) light <= ~light;
    end
endmodule
```

* Actually, our FPGAs will reset all registers to 0 when the device is programmed. But it's nice to be able to press a reset button to return to a known state rather than starting from scratch by reprogramming the device.



Clocks are fast, we're slow!

The circuit on the last slide toggles the light on every rising clock edge for which button is 1. But clocks are fast (27MHz!) and our fingers are slow, so how do we press the button for just one clock edge? Answer: we can't, but we can add some state that remembers what button was last clock cycle and then detect the clock cycles when button changes from 0 to 1.

```
module onoff_sync(input clk, reset, button,
                  output reg light);
    reg old_button; // state of button last clk
    always @ (posedge clk) begin
        if (reset)
            begin light <= 0; old_button <= 0; end
        else if (old_button==0 && button==1)
            // button changed from 0 to 1
            light <= ~light;
            old_button <= button;
        end
    endmodule
```




Asynchronous Inputs in Sequential Systems

What about external signals?



*Can't guarantee
setup and hold
times will be met!*

 When an asynchronous signal causes a setup/hold violation...





Q: Which cases are problematic?



Asynchronous Inputs in Sequential Systems

All of them can be, if more than one happens simultaneously within the same circuit.

  Guideline: ensure that external signals directly feed exactly one flip-flop




This prevents the possibility of I and II occurring in different places in the circuit, but what about metastability?



Handling Metastability

 - Preventing metastability turns out to be an impossible problem
- High gain of digital devices makes it likely that metastable conditions will resolve themselves quickly
- Solution to metastability: allow time for signals to stabilize




How many registers are necessary?

- Depends on many design parameters (clock speed, device speeds, ...)
- In 6.111, a pair of synchronization registers is sufficient



One last little problem...

 Mechanical buttons exhibit contact "bounce" when they change position, leading to multiple output transitions before finally stabilizing in the new position:



We need a debouncing circuit!

```
// Switch Debounce Module
// use your system clock for the clock input
// to produce a synchronous, debounced output
// DELAY = .01 sec with a 27Mhz clock
module debounce #(parameter DELAY=270000)
    (input reset, clock, noisy,
     output reg clean);

    reg [18:0] count;
    reg new;

    always @(posedge clock)
        if (reset) // return to known state
            begin
                count <= 0;
                new <= noisy;
                clean <= noisy;
            end
        else if (noisy != new) // input changed
            begin
                new <= noisy;
                count <= 0;
            end
        else if (count == DELAY) // stable!
            clean <= new;
        else // waiting...
            count <= count+1;

endmodule
```


On/off button: final answer

```
module onoff_sync(input clk, reset, button_in,
                  output reg light);
    // synchronizer
    reg button,btemp;
    always @(posedge clk)
        {button,btemp} <= {btemp,button_in};


    // debounce push button
    wire bpressed;
    debounce db1(.clock(clk),.reset(reset),
                .noisy(button),.clean(bpressed));

    reg old_bpressed; // state last clk cycle
    always @ (posedge clk) begin
        if (reset)
            begin light <= 0; old_bpressed <= 0; end
        else if (old_bpressed==0 && bpressed==1)
            // button changed from 0 to 1
            light <= ~light;
            old_bpressed <= bpressed;
        end
    endmodule
```

FPGA

Field Programmable Gate Array:
Set of Chips in a bread board.

Control:
Chips functions
Connections

 

A Tale of Two HDLs

VHDL

ADA-like verbose syntax, lots of redundancy (which can be good!)

Extensible types and simulation engine. Logic representations are not built in and have evolved with time (IEEE-1164).

Design is composed of entities each of which can have multiple architectures. A configuration chooses what architecture is used for a given instance of an entity.

Behavioral, dataflow and structural modeling.
Synthesizable subset...

Harder to learn and use, not technology-specific, DoD mandate

Verilog

C-like concise syntax

Built-in types and logic representations. Oddly, this led to slightly incompatible simulators from different vendors.

Design is composed of modules.

Behavioral, dataflow and structural modeling.
Synthesizable subset...

Easy to learn and use, fast simulation, good for hardware design