

www.lip.pt/~pedjor/PCLD

•State Machines

Refs:

Cyclone II device Handbook, Altera corp.

Quartus II Handbook , Altera corp.


DE2 documentation

Verilog HDL, S. Palnitkar, Prentice Hall

Sequential Logic

... Something we couldn't build with combinatorial logic

 What if you were given the following design specification:




What makes this circuit so different from those we've discussed before?

1. "State" - i.e. the circuit has memory
2. The output was changed by a input "event" (pushing a button) rather than an input "value"

Digital State

One model of what we'd like to build

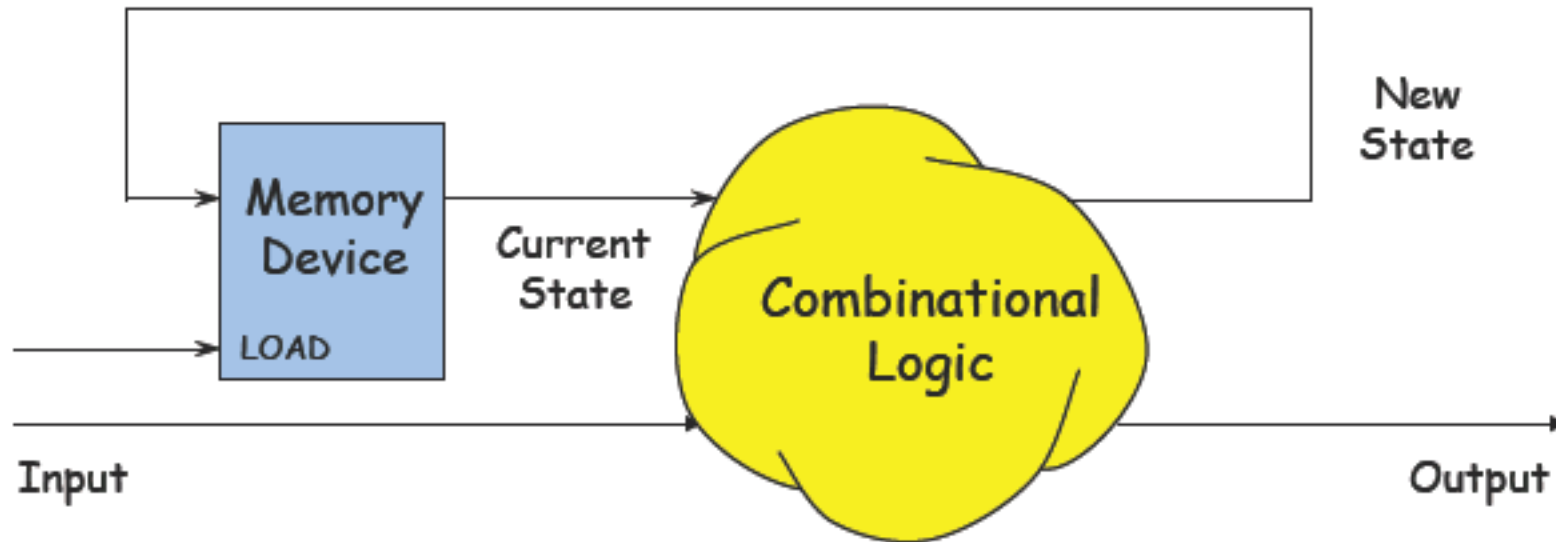


Plan: Build a Sequential Circuit with stored digital STATE -


- Memory stores CURRENT state, produced at output
- Combinational Logic computes
 - NEXT state (from input, current state)
 - OUTPUT bit (from input, current state)
- State changes on LOAD control input

When Output depends on input and current state, circuit is called a Mealy machine. If Output depends only on the current state, circuit is called a Moore machine.

Implementation for on/off button

 
 
```
module onoff(input button, output reg light);  
    always @(posedge button) light <= ~light;  
endmodule
```



Synchronous on/off button

When designing a system that accepts many inputs it would be hard to have input changes serve as the system clock (which input would we use?). So we'll use a single clock of some fixed frequency and have the inputs control what state changes happen on rising clock edges.

```
module onoff_sync(input clk, button,
                  output reg light);
    always @ (posedge clk) begin
        if (button) light <= ~light;
    end
endmodule
```



Resetting to a known state

Usually one can't rely on registers powering-on to a particular initial state*. So most designs have a RESET signal that when asserted initializes all the state to known, mutually consistent initial values.

```
module onoff_sync(input clk, reset, button,
                  output reg light);
    always @ (posedge clk) begin
        if (reset) light <= 0;
        else if (button) light <= ~light;
    end
endmodule
```

* Actually, our FPGAs will reset all registers to 0 when the device is programmed. But it's nice to be able to press a reset button to return to a known state rather than starting from scratch by reprogramming the device.



Clocks are fast, we're slow!

The circuit on the last slide toggles the light on every rising clock edge for which button is 1. But clocks are fast (27MHz!) and our fingers are slow, so how do we press the button for just one clock edge? Answer: we can't, but we can add some state that remembers what button was last clock cycle and then detect the clock cycles when button changes from 0 to 1.

```
module onoff_sync(input clk, reset, button,
                  output reg light);
    reg old_button; // state of button last clk
    always @ (posedge clk) begin
        if (reset)
            begin light <= 0; old_button <= 0; end
        else if (old_button==0 && button==1)
            // button changed from 0 to 1
            light <= ~light;
            old_button <= button;
        end
    endmodule
```



 

Asynchronous Inputs in Sequential Systems

What about external signals?



*Can't guarantee
setup and hold
times will be met!*

When an asynchronous signal causes a setup/hold violation...





Q: Which cases are problematic?



Asynchronous Inputs in Sequential Systems

All of them can be, if more than one happens simultaneously within the same circuit.

  Guideline: ensure that external signals directly feed exactly one flip-flop




This prevents the possibility of I and II occurring in different places in the circuit, but what about metastability?



Handling Metastability

 - Preventing metastability turns out to be an impossible problem
- High gain of digital devices makes it likely that metastable conditions will resolve themselves quickly
- Solution to metastability: allow time for signals to stabilize




How many registers are necessary?

- Depends on many design parameters (clock speed, device speeds, ...)
- In 6.111, a pair of synchronization registers is sufficient



One last little problem...

 Mechanical buttons exhibit contact "bounce" when they change position, leading to multiple output transitions before finally stabilizing in the new position:



We need a debouncing circuit!

```
// Switch Debounce Module
// use your system clock for the clock input
// to produce a synchronous, debounced output
// DELAY = .01 sec with a 27Mhz clock
module debounce #(parameter DELAY=270000)
    (input reset, clock, noisy,
     output reg clean);

    reg [18:0] count;
    reg new;

    always @(posedge clock)
        if (reset) // return to known state
            begin
                count <= 0;
                new <= noisy;
                clean <= noisy;
            end
        else if (noisy != new) // input changed
            begin
                new <= noisy;
                count <= 0;
            end
        else if (count == DELAY) // stable!
            clean <= new;
        else // waiting...
            count <= count+1;

endmodule
```


On/off button: final answer

```
module onoff_sync(input clk, reset, button_in,
                  output reg light);
    // synchronizer
    reg button,btemp;
    always @(posedge clk)
        {button,btemp} <= {btemp,button_in};

    // debounce push button
    wire bpressed;
    debounce db1(.clock(clk),.reset(reset),
                .noisy(button),.clean(bpressed));

    reg old_bpressed; // state last clk cycle
    always @ (posedge clk) begin
        if (reset)
            begin light <= 0; old_bpressed <= 0; end
        else if (old_bpressed==0 && bpressed==1)
            // button changed from 0 to 1
            light <= ~light;
            old_bpressed <= bpressed;
        end
    endmodule
```

A Simple problem...

 

```
always @ (posedge button)
begin
    led<=~led;
end
```

A Simple problem...



Question #1:

If the button has a value “low” the led should be ‘ON” or “OFF” ?

Question #2:

If the button has a value “high” the led should be ‘ON” or “OFF” ?

Question #3:

If the button is pressed the led should be ‘ON” or “OFF” ?

Depends on the
STATE!!

This is a
State machine!!




A Simple problem...



Let's implement a state machine for this simple problem




State Diagram:

 


State Machines

Can get complicated...

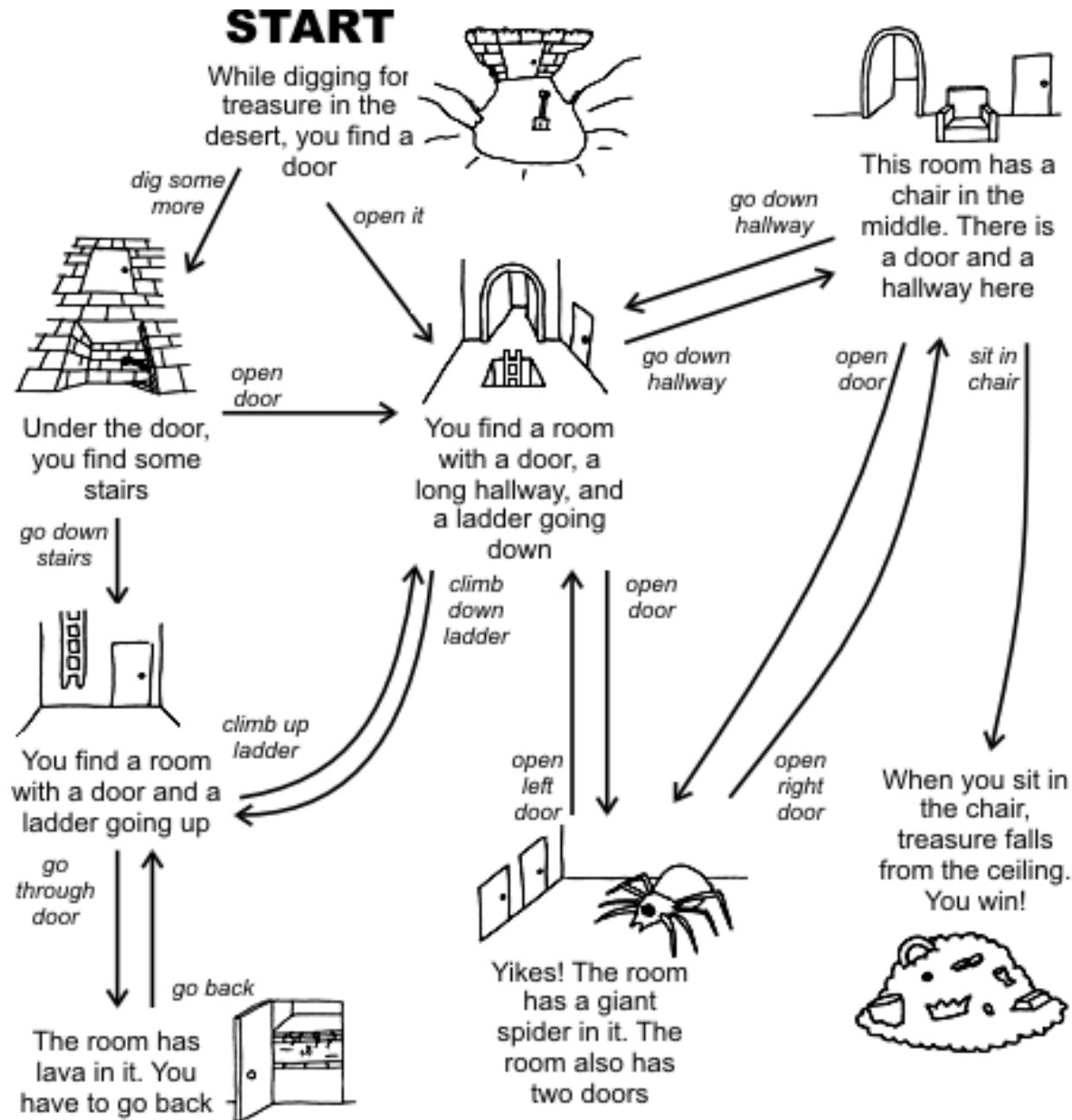


The worst one!!

 


Finite State Machines

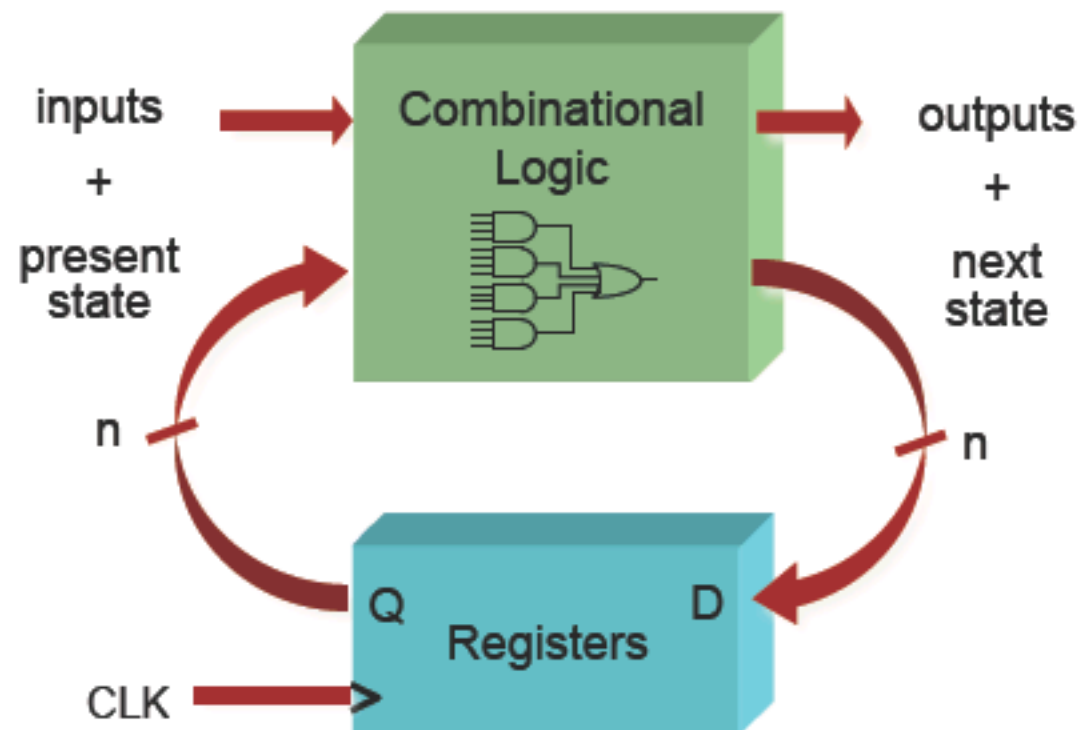- Finite State Machines (FSMs) are a useful abstraction for *sequential circuits* with centralized "*states*" of operation
- At each clock edge, combinational logic computes *outputs* and *next state* as a function of *inputs* and *present state*




Design Example: Level-to-Pulse

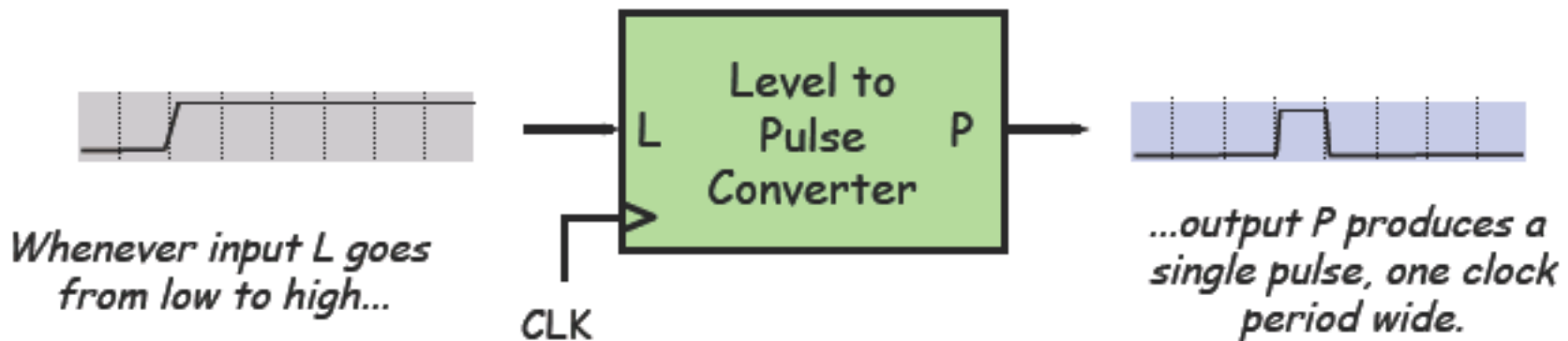- A **level-to-pulse converter** produces a single-cycle pulse each time its input goes high.
- It's a synchronous rising-edge detector.
- Sample uses:
 - Buttons and switches pressed by humans for arbitrary periods of time
 - Single-cycle enable signals for counters




Step 1: State Transition Diagram

- Block diagram of desired system:

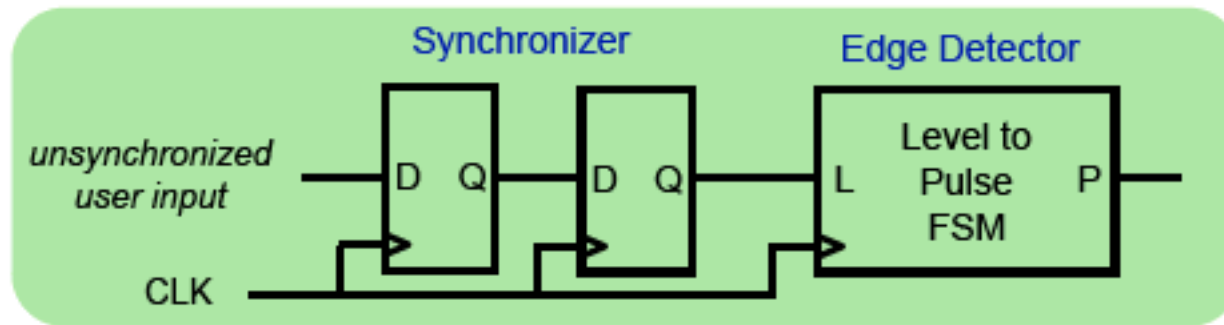

 - State transition diagram** is a useful FSM representation and design aid:



In each state there should be one and only one arc for each input combination₂₁

Choosing State Representation

Choice #1: binary encoding

For N states, use $\text{ceil}(\log_2 N)$ bits to encode the state with each state represented by a unique combination of the bits.

Tradeoffs: most efficient use of state registers, but requires more complicated combinational logic to detect when in a particular state.


Choice #2: "one-hot" encoding

For N states, use N bits to encode the state where the bit corresponding to the current state is 1, all the others 0.

Tradeoffs: more state registers, but often much less combinational logic since state decoding is trivial.


Step 2: Logic Derivation

 Transition diagram is readily converted to a state transition table (just a truth table)




Current State		In	Next State		Out
S_1	S_0	L	S_1^+	S_0^+	P
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	1
1	1	0	0	0	0
1	1	1	1	1	0

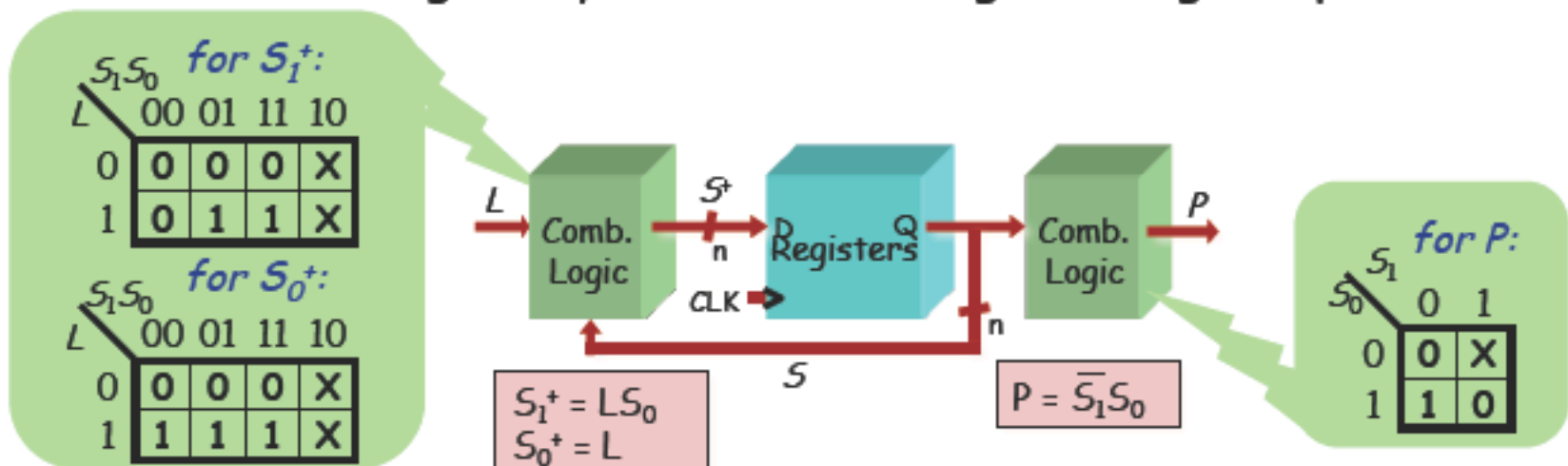
- Combinational logic may be derived using Karnaugh maps




Moore Level-to-Pulse Converter

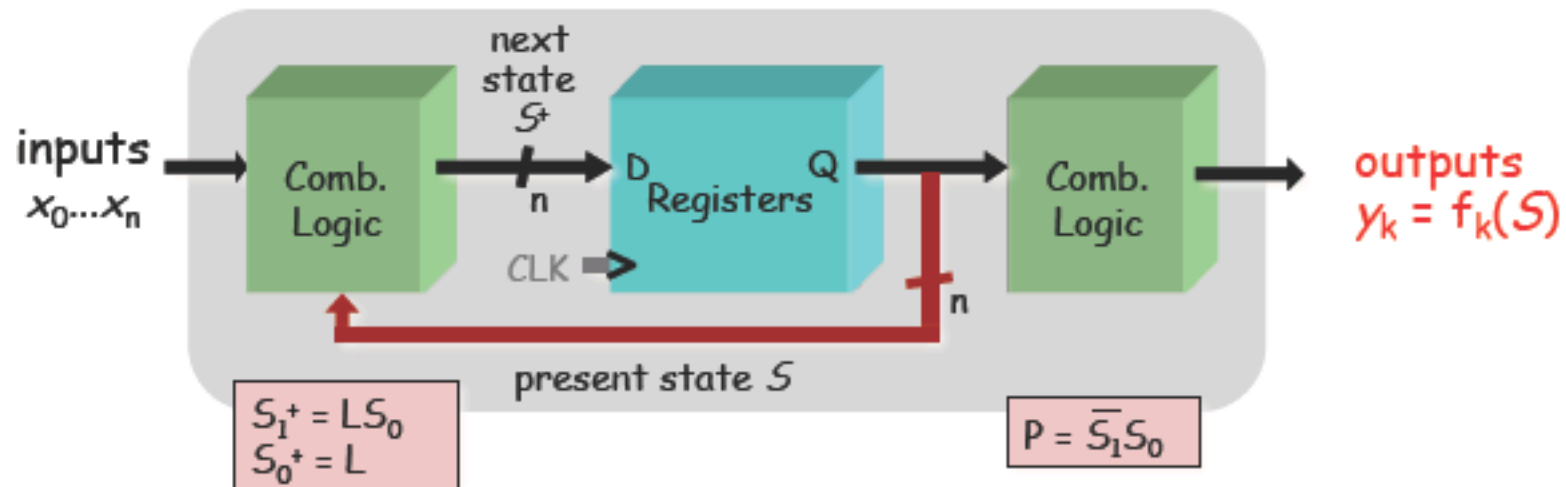

 Moore FSM circuit implementation of level-to-pulse converter:



 

FSM Example


GOAL:

Build an electronic combination lock with a reset button, two number buttons (0 and 1), and an unlock output. The combination should be **01011**.





STEPS:

 1. Design lock FSM (block diagram, state transitions)
2. Write Verilog module(s) for FSM





Step 1A: Block Diagram

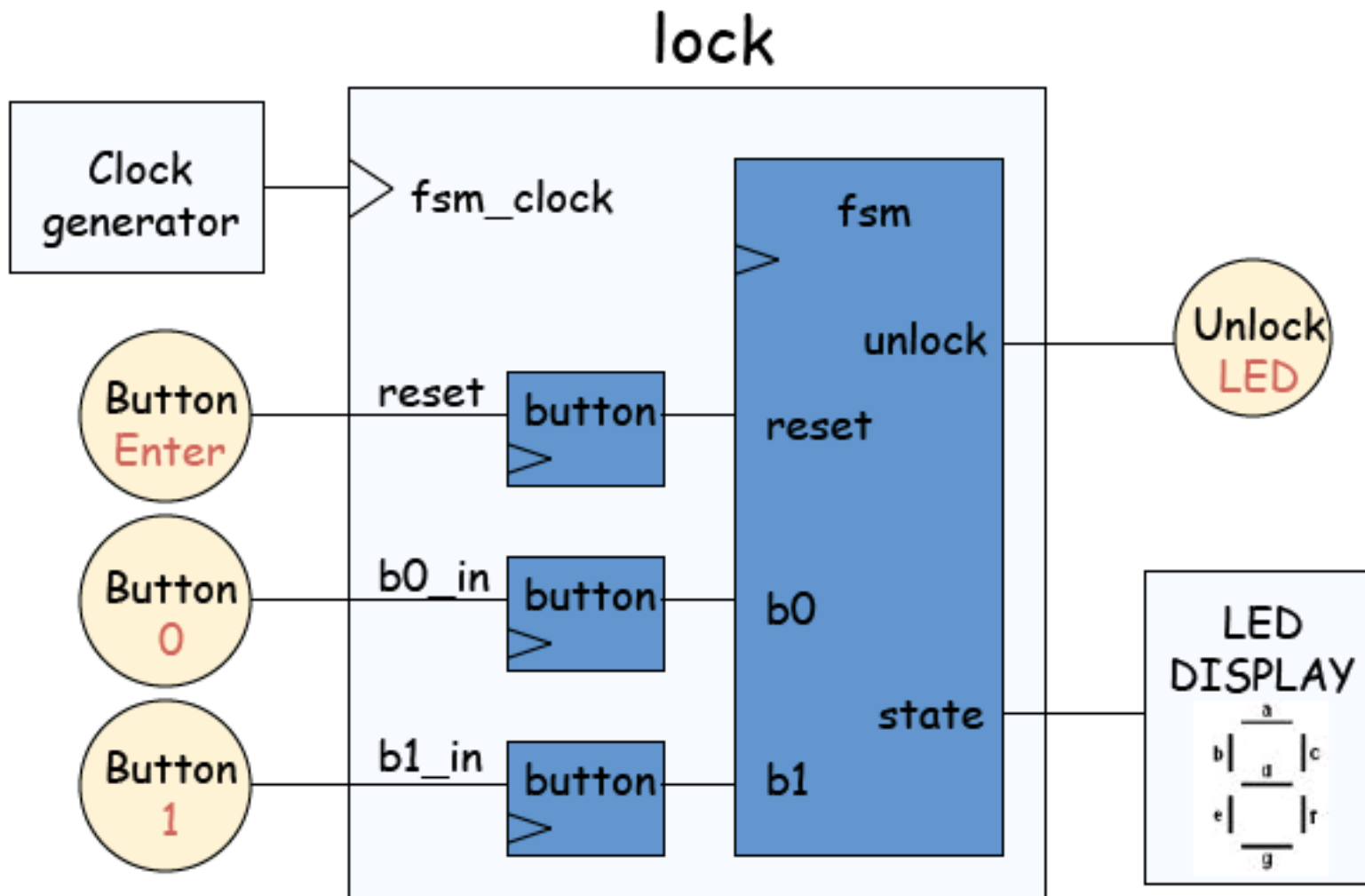

 

Step 1B: State transition diagram

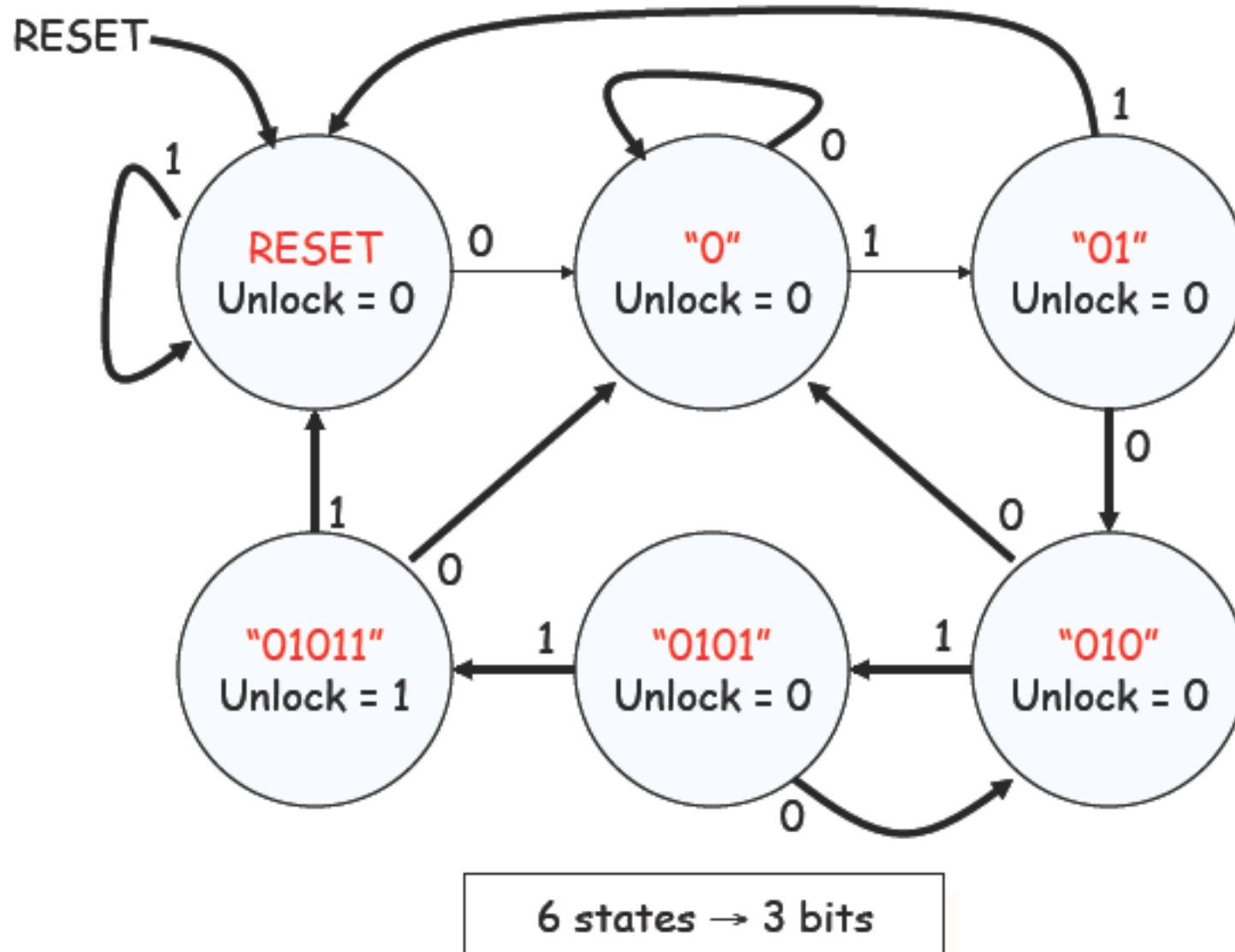

 

Step 2: Write Verilog

```
module lock(input clk,reset_in,b0_in,b1_in,  
            output out);
```

```
    // synchronize push buttons, convert to pulses
```

```
    // implement state transition diagram
```

```
    reg [2:0] state,next_state;
```

```
    always @(*) begin
```

```
        // combinational logic!
```

```
        next_state = ???;
```

```
    end
```


```
    always @(posedge clk) state <= next_state;
```

```
    // generate output
```

```
    assign out = ???;
```

```
    // debugging?
```

```
endmodule
```

 


Step 2A: Synchronize buttons

```
// button
// push button synchronizer and level-to-pulse converter
// OUT goes high for one cycle of CLK whenever IN makes a
// low-to-high transition.
```

```
module button(
    input clk, in,
    output out
);
    reg r1, r2, r3;
    always @(posedge clk)
    begin
        r1 <= in;      // first reg in synchronizer
        r2 <= r1;      // second reg in synchronizer, output is in sync!
        r3 <= r2;      // remembers previous state of button
    end
```
 
```
    // rising edge = old value is 0, new value is 1
    assign out = ~r3 & r2;
endmodule
```



Step 2B: state transition diagram

```
parameter S_RESET = 0; // state assignments
parameter S_0 = 1;
parameter S_01 = 2;
parameter S_010 = 3;
parameter S_0101 = 4;
parameter S_01011 = 5;
```

```
reg [2:0] state, next_state;
always @(*) begin
```

```
    // implement state transition diagram
```

```
    if (reset) next_state = S_RESET;
```

```
    else case (state)
```

```
        S_RESET: next_state = b0 ? S_0      : (b1 ? S_RESET : state);
```

```
        S_0:      next_state = b0 ? S_0      : (b1 ? S_01    : state);
```

```
        S_01:     next_state = b0 ? S_010    : (b1 ? S_RESET : state);
```

```
        S_010:    next_state = b0 ? S_0      : (b1 ? S_0101  : state);
```

```
        S_0101:   next_state = b0 ? S_010    : (b1 ? S_01011 : state);
```


```
        S_01011:  next_state = b0 ? S_0      : (b1 ? S_RESET : state);
```


```
        default:  next_state = S_RESET; // handle unused states
```

```
    endcase
```

```
end
```
 
```
always @(posedge clk) state <= next_state;
```



 

Step 2C: generate output

```
// it's a Moore machine! Output only depends on current state  
assign out = (state == S_01011);
```

Step 2D: debugging?

```
// hmmm. What would be useful to know? Current state?  
assign hex_display = {1'b0,state[2:0]};
```



Step 2: final Verilog implementation

```
module lock(input clk,reset_in,b0_in,b1_in,
            output out, output [3:0] hex_display);

    wire reset, b0, b1; // synchronize push buttons, convert to pulses
    button b_reset(clk,reset_in,reset);
    button b_0(clk,b0_in,b0);
    button b_1(clk,b1_in,b1);

    parameter S_RESET = 0; parameter S_0 = 1; // state assignments
    parameter S_01 = 2; parameter S_010 = 3;
    parameter S_0101 = 4; parameter S_01011 = 5;

    reg [2:0] state,next_state;
    always @(*) begin // implement state transition diagram
        if (reset) next_state = S_RESET;
        else case (state)
            S_RESET: next_state = b0 ? S_0 : (b1 ? S_RESET : state);
            S_0:      next_state = b0 ? S_0 : (b1 ? S_01 : state);
            S_01:     next_state = b0 ? S_010 : (b1 ? S_RESET : state);
            S_010:    next_state = b0 ? S_0 : (b1 ? S_0101 : state);
            S_0101:   next_state = b0 ? S_010 : (b1 ? S_01011 : state);
            S_01011:  next_state = b0 ? S_0 : (b1 ? S_RESET : state);
            default:  next_state = S_RESET; // handle unused states
        endcase
    end
    always @(posedge clk) state <= next_state;

    assign out = (state == S_01011); // assign output: Moore machine
    assign hex_display = {1'b0,state}; // debugging
endmodule
```


Partitioning state machines


Basically the trick is that you need to put the top one on hold

Partitioning state machines

Basically the trick is that you need to put the top one on hold


Toward FSM Modularity

- Consider the following abstract FSM:

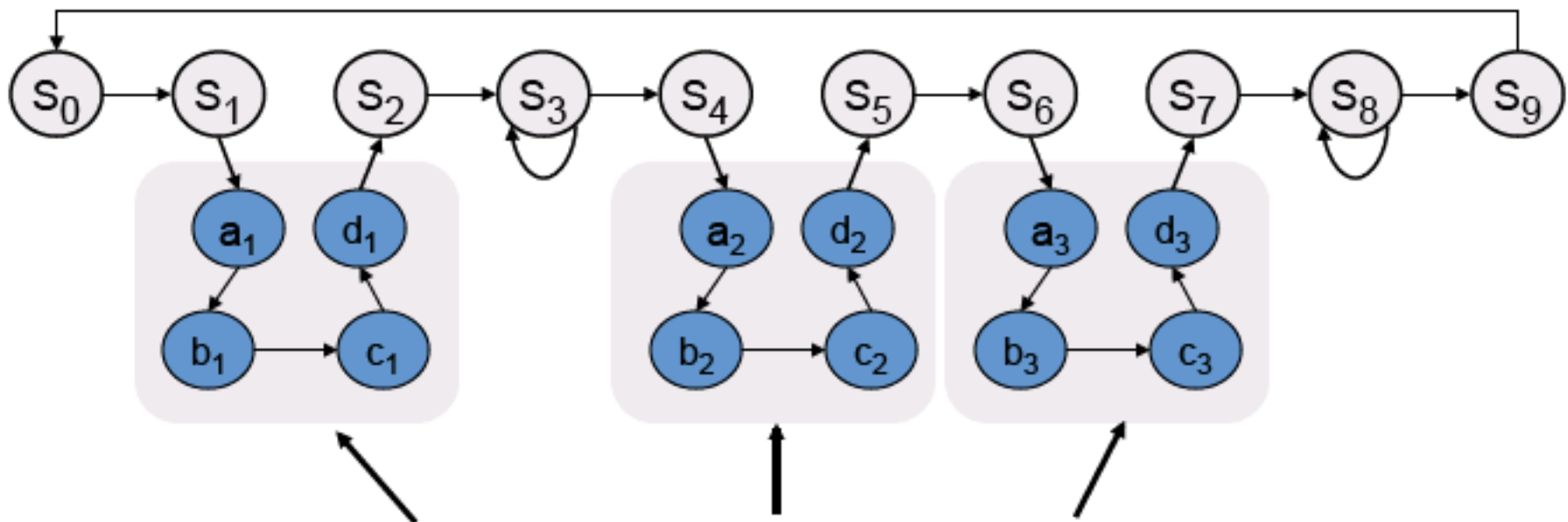


- Suppose that each set of states $a_x \dots d_x$ is a "sub-FSM" that produces exactly the same outputs.
- Can we simplify the FSM by removing equivalent states?
No! The outputs may be the same, but the next-state transitions are not.
- This situation closely resembles a **procedure call** or **function call** in software...how can we apply this concept to FSMs?

The Major/Minor FSM Abstraction

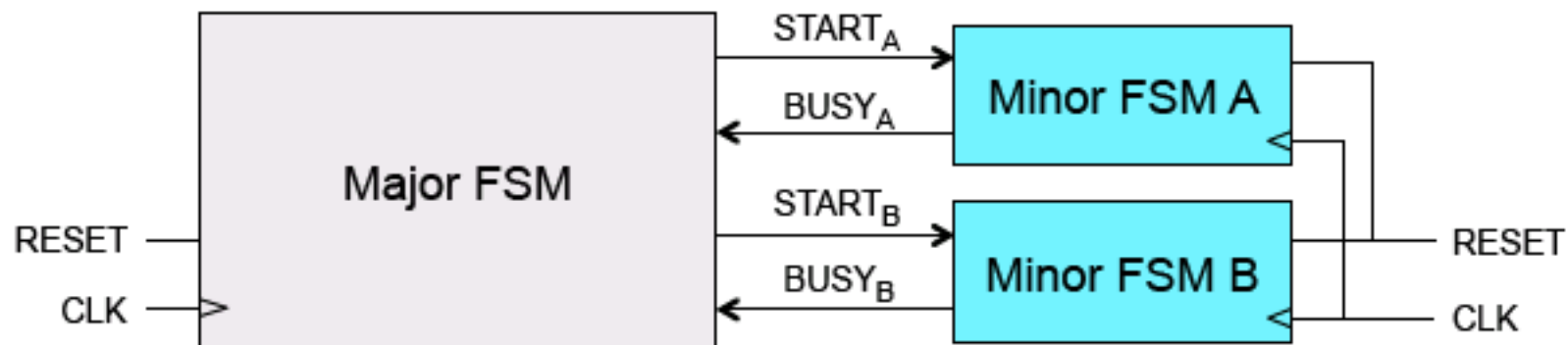

- Subtasks are encapsulated in **minor FSMs** with common reset and clock
- Simple communication abstraction:
 - **START**: tells the minor FSM to begin operation (the call)
 - **BUSY**: tells the major FSM whether the minor is done (the return)
- The major/minor abstraction is great for...
 - Modular designs (*always* a good thing)
 - Tasks that occur often but in different contexts
 - Tasks that require a variable/unknown period of time
 - Event-driven systems


Inside the Major FSM

 

1. Wait until the minor FSM is ready

2. Trigger the minor FSM (and make sure it's started)



3. Wait until the minor FSM is done

 

Variations:


- Usually don't need both Step 1 and Step 3
- One cycle "done" signal instead of multi-cycle "busy"

Inside the Minor FSM

 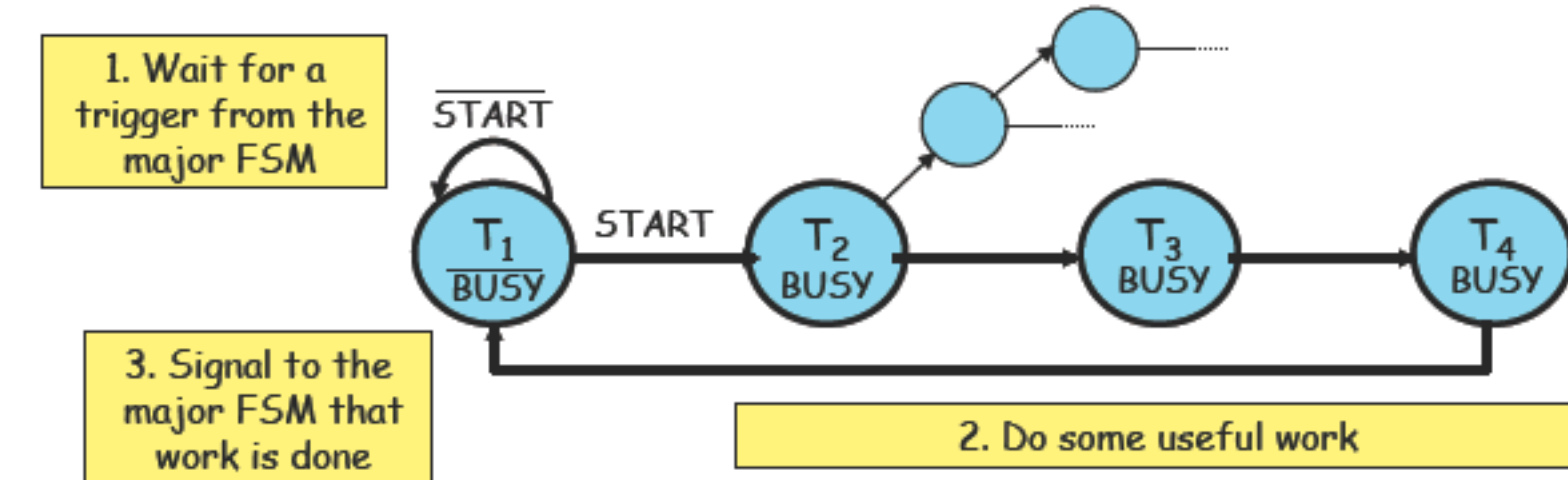


Optimizing the Minor FSM

 Good idea: de-assert BUSY one cycle early




Bad idea #1:

T_4 may not immediately return to T_1


 


Bad idea #2:



BUSY never asserts!

 

A Four-FSM Example

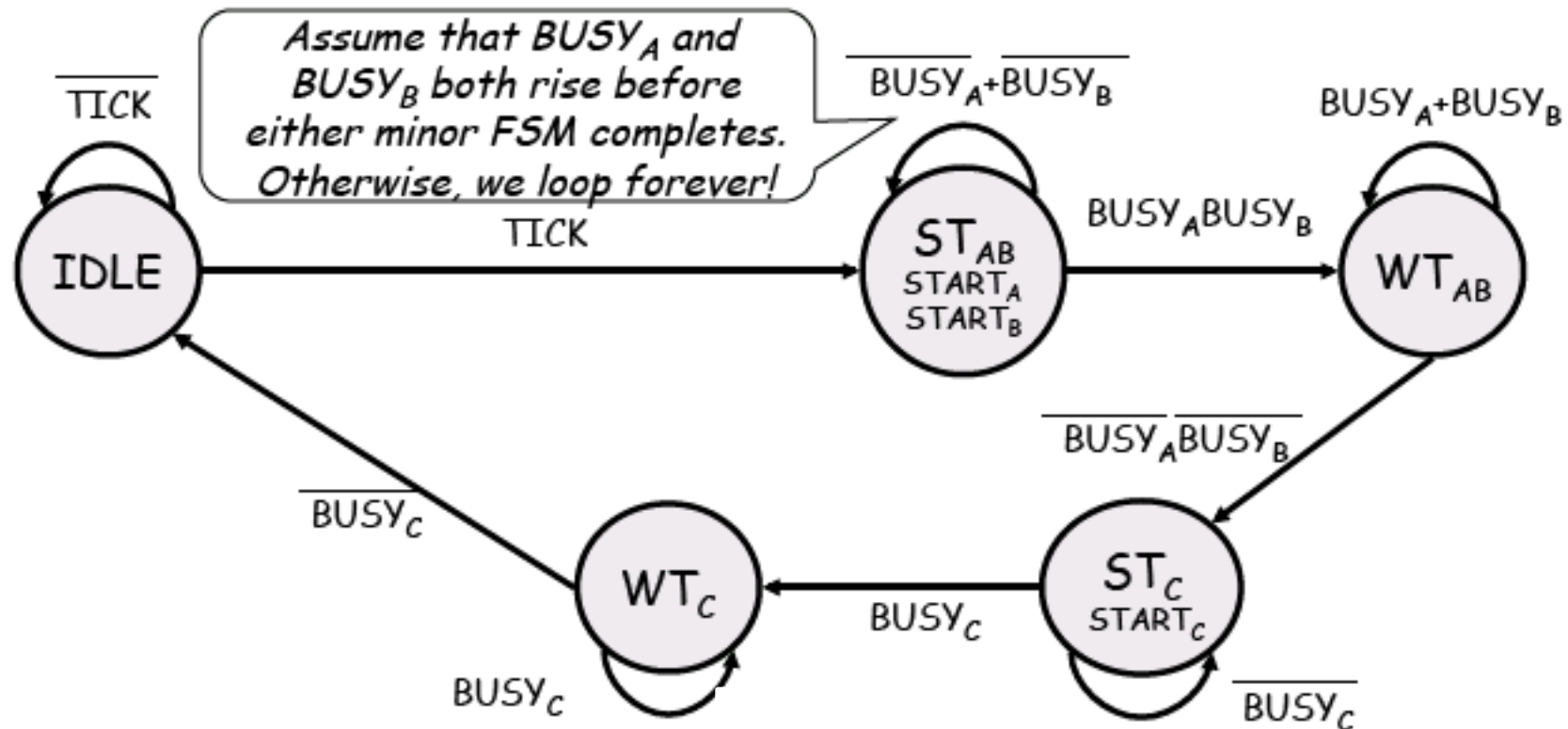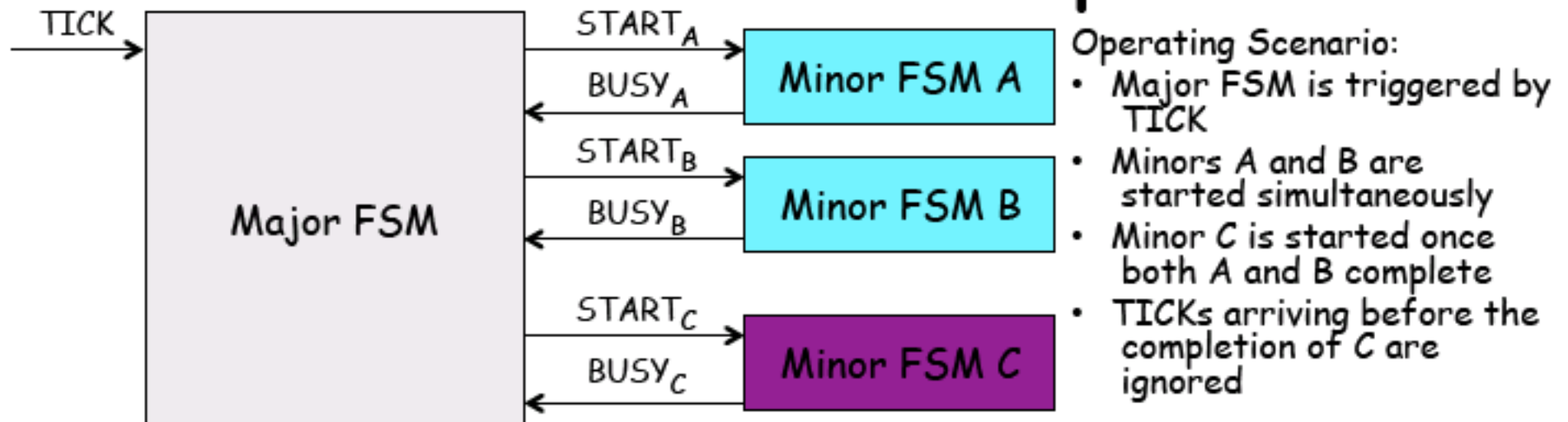

Four-FSM Sample Waveform

 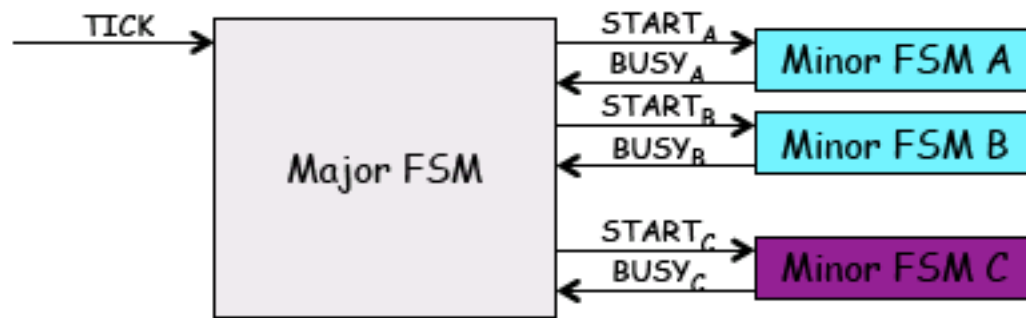

How to write a state machine in verilog

```
input k1, k2, k3, clk;
output l1, l2, l3;

//create registers
//to "store state"
reg [3:0] state, next;
```

```
//use parameters to give names
//to states
```

```
parameter s1=0;
parameter s2=1;
parameter s3=2;
parameter s4=3;
```

```
//The core code
//this, and only this,
//changes the states
always @ (posedge clk)
    state<=next;
```

```
//decide which will be
//the next state
```

```
always @ (state or k1 or k2 or k3)
case (state)
    S1:
        if(????) next=????;
        else next=S1;
    S2:
        if(????) next=????;
        else next=S2; //The wait modes
    S3:
        if(????) next=????;
        else next=S3;
```

```
//compute output
//according to state and/or input
assign l1= S1;
assign l2=S2 || S3;
assign l3=S3;
```

A vending machine

- All selections are \$0.30.
- The machine makes change. (Dimes and nickels only.)
- Inputs: limit 1 per clock
 - Q - quarter inserted
 - D - dime inserted
 - N - nickel inserted
- Outputs: limit 1 per clock
 - DC - dispense can
 - DD - dispense dime
 - DN - dispense nickel



What states?



- A starting (idle) state:

idle

- A state for each possible amount of money captured:

got5c

got10c

got15c

...

- What's the maximum amount of money captured before purchase?

25 cents (just shy of a purchase) + one quarter (largest coin)

...

got35c

got40c

got45c

got50c

- States to dispense change (one per coin dispensed):

got45c


Dispense
Dime

Dispense
Nickel

A Moore vender

Here's a first cut at the state transition diagram.

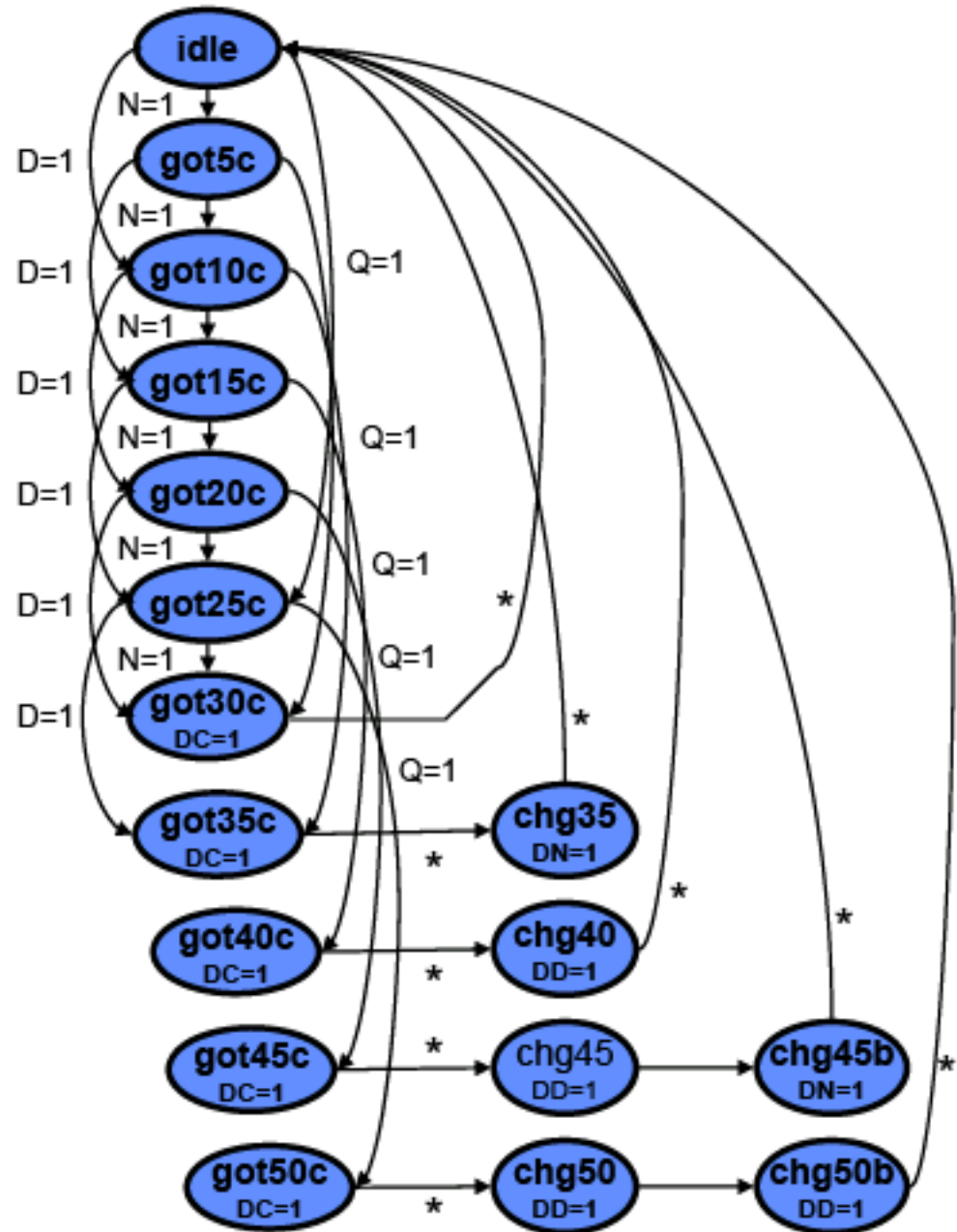See a better way?
So do we.
Don't go away...





State reduction



Duplicate states have:


- The same outputs, and
- The same transitions

 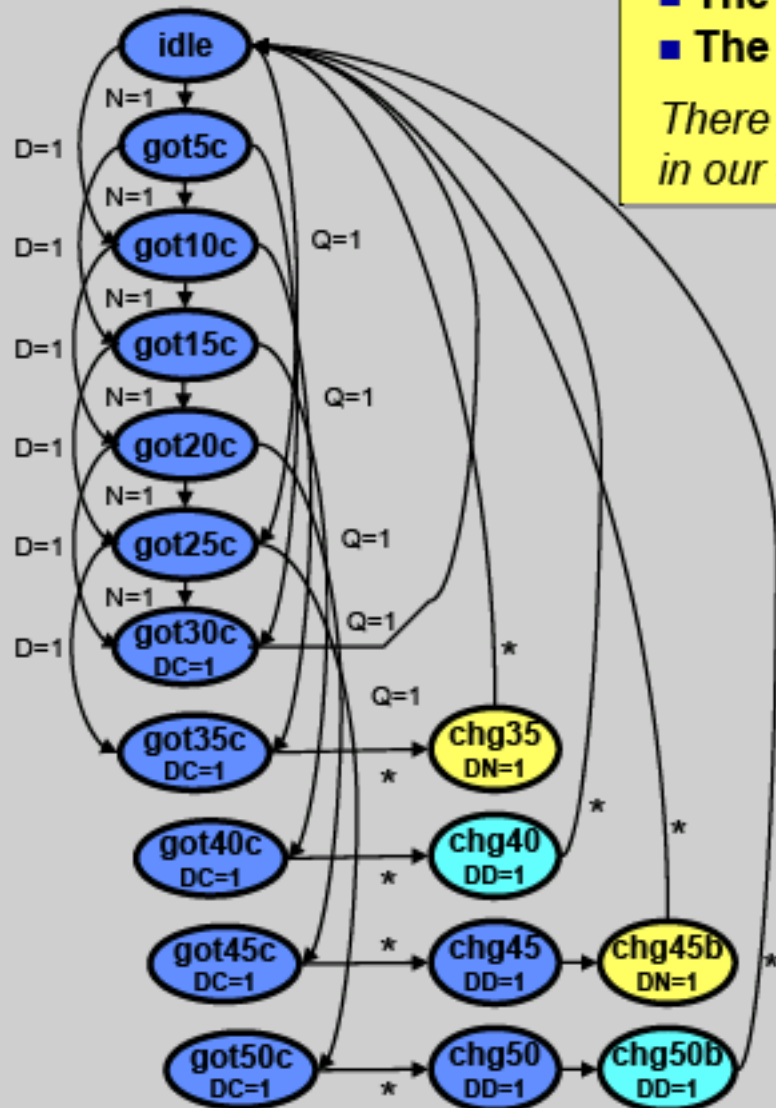There are two duplicates in our original diagram.




17 states
5 state bits

15 states
4 state bits

 

The verilog code

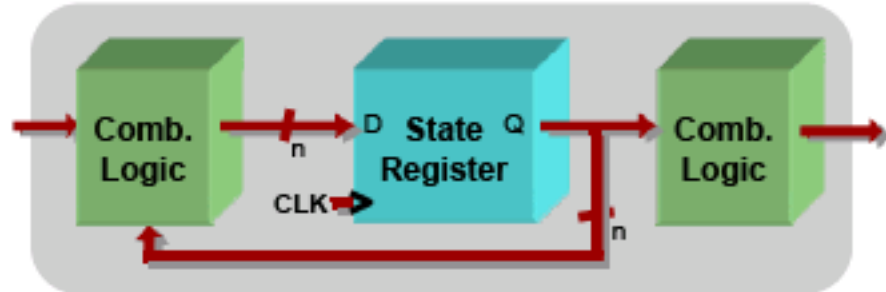

***FSMs are easy in Verilog.
Simply write one of each:***

- **State register**
(sequential always block)
- **Next-state**
combinational logic
(comb. always block with `case`)
- **Output combinational**
logic block
(comb. always block or `assign` statements)

```
module mooreVender (N, D, Q, DC, DN, DD,  
                    clk, reset, state);  
    input N, D, Q, clk, reset;  
    output DC, DN, DD;  
    output [3:0] state;  
    reg [3:0] state, next;
```

States defined with `parameter` keyword

```
    parameter IDLE = 0;  
    parameter GOT_5c = 1;  
    parameter GOT_10c = 2;  
    parameter GOT_15c = 3;  
    parameter GOT_20c = 4;  
    parameter GOT_25c = 5;  
    parameter GOT_30c = 6;  
    parameter GOT_35c = 7;  
    parameter GOT_40c = 8;  
    parameter GOT_45c = 9;  
    parameter GOT_50c = 10;  
    parameter RETURN_20c = 11;  
    parameter RETURN_15c = 12;  
    parameter RETURN_10c = 13;  
    parameter RETURN_5c = 14;
```

**State register defined with sequential
always block**

```
    always @ (posedge clk or negedge reset)  
        if (!reset)    state <= IDLE;  
        else            state <= next;
```




The Verilog code

Next-state logic within a combinational **always** block

```
always @ (state or N or D or Q) begin

    case (state)
        IDLE:      if (Q) next = GOT_25c;
                   else if (D) next = GOT_10c;
                   else if (N) next = GOT_5c;
                   else next = IDLE;

        GOT_5c:    if (Q) next = GOT_30c;
                   else if (D) next = GOT_15c;
                   else if (N) next = GOT_10c;
                   else next = GOT_5c;

        GOT_10c:   if (Q) next = GOT_35c;
                   else if (D) next = GOT_20c;
                   else if (N) next = GOT_15c;
                   else next = GOT_10c;

        GOT_15c:   if (Q) next = GOT_40c;
                   else if (D) next = GOT_25c;
                   else if (N) next = GOT_20c;
                   else next = GOT_15c;

        GOT_20c:   if (Q) next = GOT_45c;
                   else if (D) next = GOT_30c;
                   else if (N) next = GOT_25c;
                   else next = GOT_20c;
```

```
GOT_25c:  if (Q) next = GOT_50c;
           else if (D) next = GOT_35c;
           else if (N) next = GOT_30c;
           else next = GOT_25c;
```

```
GOT_30c:  next = IDLE;
GOT_35c:  next = RETURN_5c;
GOT_40c:  next = RETURN_10c;
GOT_45c:  next = RETURN_15c;
GOT_50c:  next = RETURN_20c;
```

```
RETURN_20c: next = RETURN_10c;
RETURN_15c: next = RETURN_5c;
RETURN_10c: next = IDLE;
RETURN_5c:  next = IDLE;
```

```
default: next = IDLE;
endcase
```




```
end
```

Combinational output assignment

```
assign DC = (state == GOT_30c || state == GOT_35c ||
             state == GOT_40c || state == GOT_45c ||
             state == GOT_50c);
assign DN = (state == RETURN_5c);
assign DD = (state == RETURN_20c || state == RETURN_15c ||
             state == RETURN_10c);
```

```
endmodule
```

Clocking

   


Where should CLK come from?


- Option 1: external crystal
 - Stable, known frequency, typically 50% duty cycle
- Option 2: internal signals
 - Option 2A: output of combinational logic



 
- No! If inputs to logic change, output may make several transitions before settling to final value → several rising edges, not just one! Hard to design away output glitches...
- Option 2B: output of a register
 - Okay, but timing of CLK2 won't line up with CLK1




Clocking in and ideal world

 


Ideal world:

 

Clocking in a not so perfect reality

 

Real world has clock skew:

 

FPGAs contain global
clock lines that have
low skew. Number is
limited

Clocks with periods multiple of two

```
reg clk2,clk4,clk8,clk16;  
always @(posedge clk) clk2 <= ~clk2;  
always @(posedge clk2) clk4 <= ~clk4;  
always @(posedge clk4) clk8 <= ~clk8;  
always @(posedge clk8) clk16 <= ~clk16;
```




Solution: 1 clock, many enables

Use one (high speed) clock, but create enable signals to select a subset of the edges to use for a particular piece of sequential logic


```
reg [3:0] count;  
always @(posedge clk) count <= count + 1; // counts 0..15  
wire enb2 = (count[0] == 1'b1);  
wire enb4 = (count[1:0] == 2'b11);  
wire enb8 = (count[2:0] == 3'b111);  
wire enb16 = (count[3:0] == 4'b1111);
```
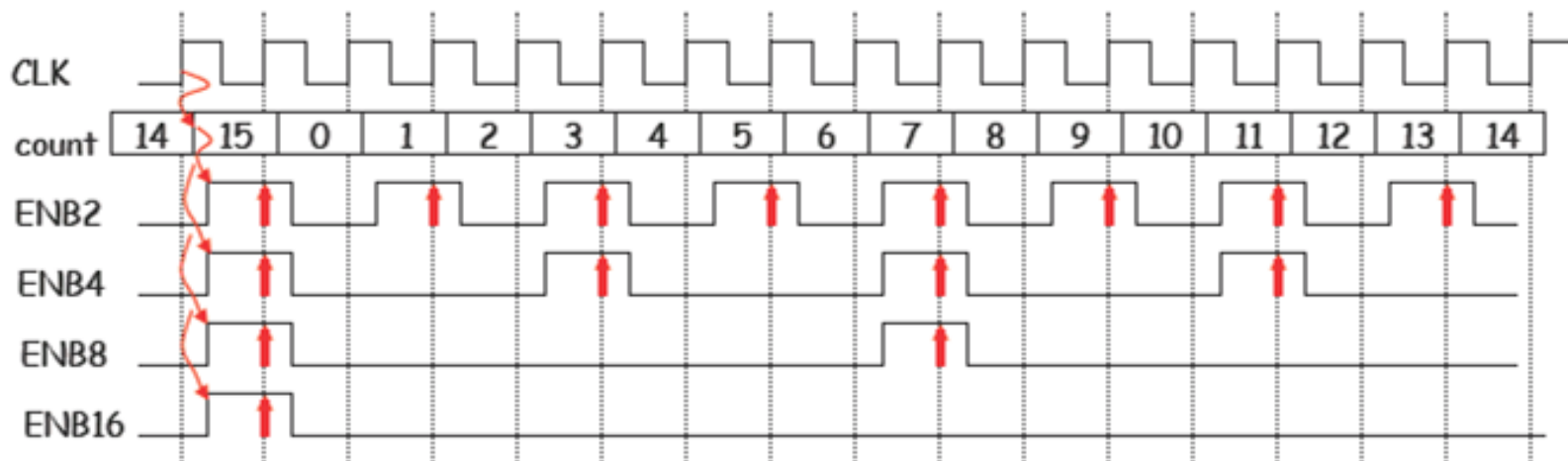
```
always @(posedge clk)  
if (enb2) begin  
    // get here every 2nd cycle  
end
```



↑ = clock edge selected by enable signal

The Phase Locked Loop (PLL)

 

A feature available in Cyclone II devices that employs a phase-locked loop (PLL). The Cyclone II PLL provides advanced multiplication, programmable duty cycle, phase shifting, programmable bandwidth, manual clock switchover, clock outputs driving all networks, and a source synchronous mode.


You can take advantage of the Cyclone II PLL with the [altpll megafunction](#).

Phase-Locked Loops (ALTPLL)

Megafunction User Guide

TOOLS

File→new→statemachine

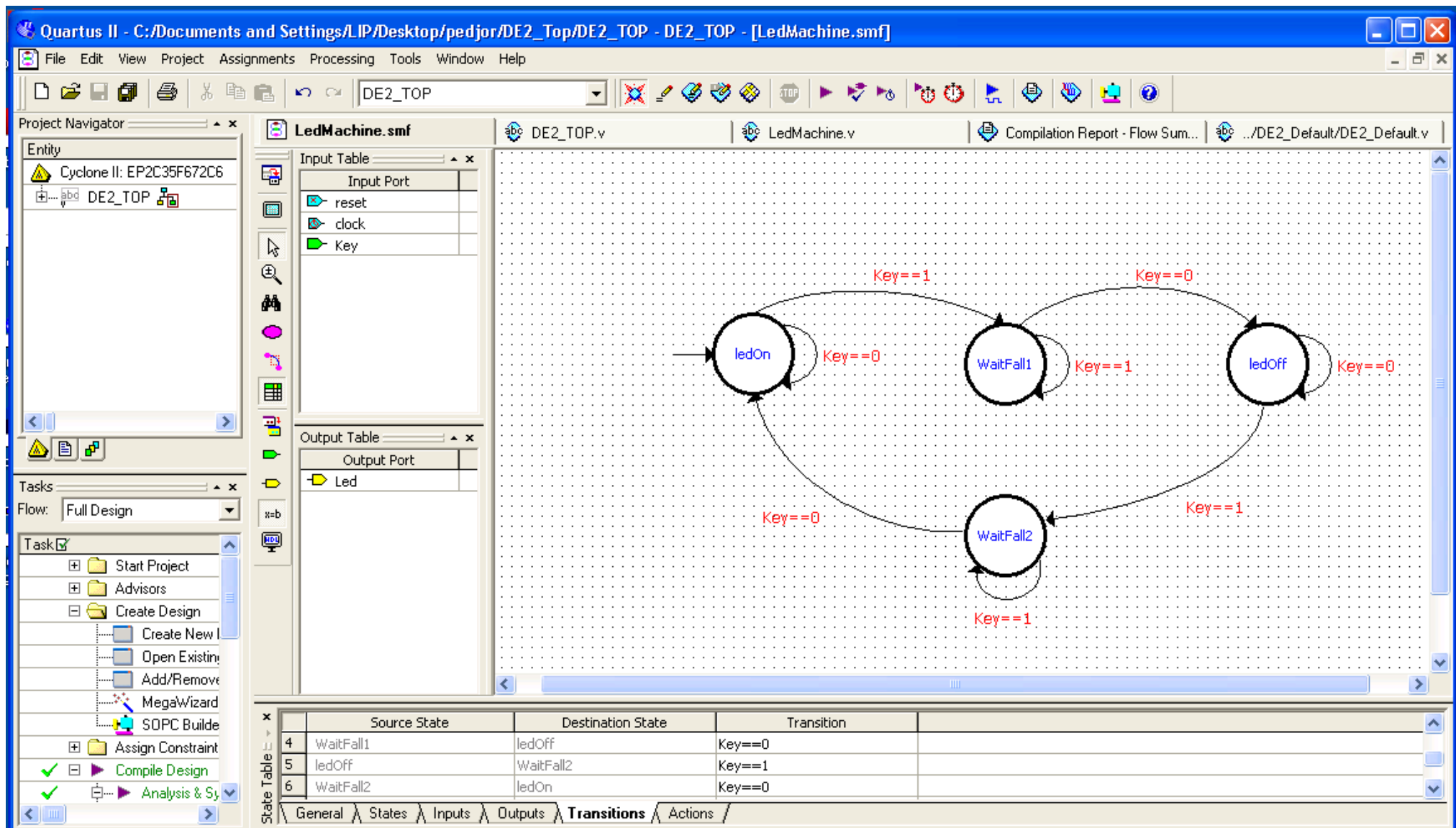

For more information about creating and editing state machine diagrams, refer to the Quartus II Help.

Define the states output

Quartus II - C:/Documents and Settings/LIP/Desktop/pedjor/DE2_Top/DE2_TOP - DE2_TOP - [LedMachine.smf]

File Edit View Project Assignments Processing Tools Window Help

DE2_TOP

Project Navigator

Entity

- Cyclone II: EP2C35F672C6
- DE2_TOP

Tasks

Flow: Full Design

Task

- Start Project
- Advisors
- Create Design
 - Create New I
 - Open Existin
 - Add/Remove
 - MegaWizard
 - SOPC Build
- Assign Constraint
- Compile Design
- Analysis & Sy

LedMachine.smf

DE2_TOP.v

LedMachine

Input Table

Input Port
reset
clock
Key

Output Table

Output Port
Led

State Properties

General Incoming Transitions Outgoing Transitions Actions Format

Output Port	Output Value	Additional Conditions
Led		
<< new >>		

OK Cancel

ledOn

Key==0

Key==1

State Table

Source State	Destination State	Transition
ledOn	ledOn	Key==0
WaitFall1	WaitFall1	Key==1
ledOn	WaitFall1	Key==1

General States Inputs Outputs Transitions Actions

Type Message

Info: Device 1 contains JTAG ID code 0x020B40DD

Quartus II - C:/Documents and Settings/LIP/Desktop/pedjor/DE2_Top/DE2_Top - DE2_Top - [LedMachine.smf]

File Edit View Project Assignments Processing Tools Window Help

DE2_Top

Project Navigator

Entity

- Cyclone II: EP2C35F672C6
- DE2_Top

Tasks

Flow: Full Design

Task

- Start Project
- Advisors
- Create Design
 - Create New I
 - Open Existing
 - Add/Remove
 - MegaWizard
 - SOPC Builder
- Assign Constraint
- Compile Design
- Analysis & Synthesis

LedMachine.smf

Input Table

Input Port
reset
clock
Key

Output Table

Output Port
Led

DE2_Top.v

LedMachine.v

Compilation Report - Flow Sum...

../DE2_Default/DE2_Default.v

State Table

	Source State	Destination State	Equation
1	ledOn	ledOn	Key==0
2	WaitFall1	WaitFall1	Key==1
3	ledOn	WaitFall1	Key==1

General States Inputs Outputs Transitions Actions

Transition Properties

Source state: ledOn

Destination state: WaitFall1

Equation: Key==1

☐ Use VHDL 'OTHERS' transition.

Note: The VHDL 'OTHERS' transition is used when none of the outgoing transitions from the state are true.

OK Cancel

Messages

Type	Message
Info	Info: Device 1 contains JTAG ID code 0x020B40DD
Info	Info: Configuration succeeded -- 1 device(s) configured
Info	Info: Successfully performed operation(s)
Info	Info: Ended Programmer operation at Tue Mar 17 14:16:59 2009

System (20) Processing (195) Extra Info Info (51) Warning (144) Critical Warning Error Sup

Message: 0 of 20


Location:

For Help, press F1

298, 62

Idle

5

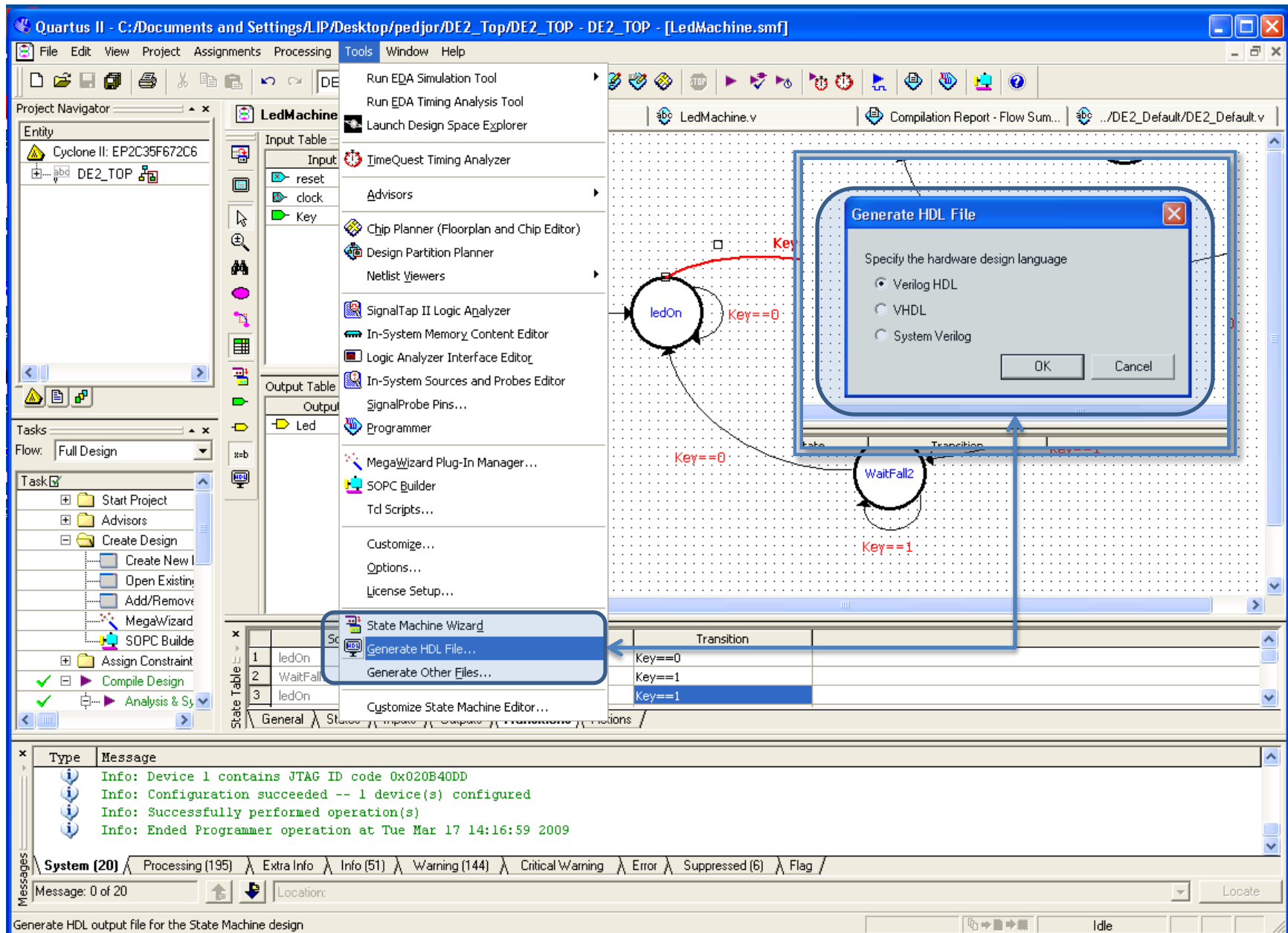

The “LedMachine” module

The screenshot displays the Quartus II software interface. The title bar indicates the project path: `C:/Documents and Settings/LIP/Desktop/pedjor/DE2_Top/DE2_TOP - DE2_TOP - [LedMachine.v]`. The main window shows the Verilog code for the `LedMachine` module. The code is as follows:

```
22 module LedMachine (  
23     reset, clock, Key,  
24     Led);  
25  
26     input reset;  
27     input clock;  
28     input Key;  
29     tri0 reset;  
30     tri0 Key;  
31     output Led;  
32     reg Led;  
33     reg [3:0] fstate;  
34     reg [3:0] reg_fstate;  
35     parameter ledOn=0, WaitFall1=1, ledOff=2, WaitFall2=3;  
36  
37     always @ (posedge clock)  
38     begin  
39         if (clock) begin  
40             fstate <= reg_fstate;  
41         end  
42     end  
43  
44     always @ (fstate or reset or Key)  
45     begin  
46         if (reset) begin  
47             reg_fstate <= ledOn;  
48             Led <= 1'b0;  
49         end  
50         else begin  
51             Led <= 1'b0;  
52             case (fstate)  
53                 ledOn: begin
```

The interface includes a Project Navigator on the left showing the project hierarchy, a Tasks pane with a list of tasks, and a Messages pane at the bottom. The Messages pane shows a tab for 'System' with various message categories like Processing, Extra Info, Info, Warning, Critical Warning, Error, Suppressed, and Flag. The status bar at the bottom indicates 'Ln 1, Col 1' and 'Idle'.

The top design

Quartus II - C:/Documents and Settings/LIP/Desktop/pedjor/DE2_Top/DE2_TOP - DE2_TOP - [DE2_TOP.v]

File Edit View Project Assignments Processing Tools Window Help

DE2_TOP

Project Navigator

Entity

Cyclone II: EP2C35F672C6

DE2_TOP

Tasks

Flow: Full Design

Task

Start Project

Advisors

Create Design

Create New I

Open Existing

Add/Remove

MegaWizard

SOPC Builder

Assign Constraint

Compile Design

Analysis & Syn

```
310 assign LEDR[17:3] = 15'h3FFFF;
311 assign LCD_ON = 1'b1;
312 assign LCD_BLON = 1'b1;
313
314 // All inout port turn to tri-state
315 assign DRAM_DQ = 16'hzzzz;
316 assign FL_DQ = 8'hzz;
317 assign SRAM_DQ = 16'hzzzz;
318 assign OTG_DATA = 16'hzzzz;
319 assign LCD_DATA = 8'hzz;
320 assign SD_DAT = 1'bz;
321 assign I2C_SDAT = 1'bz;
322 assign ENET_DATA = 16'hzzzz;
323 assign AUD_ADCLRCK = 1'bz;
324 assign AUD_DACLRCK = 1'bz;
325 assign AUD_BCLK = 1'bz;
326 assign GPIO_0 = 36'hzzzzzzzz;
327 assign GPIO_1 = 36'hzzzzzzzz;
328
329 //LedMachine Maq(KEY[0],CLOCK_50,KEY[1],LEDG[0]);
330
331 assign LEDR[0]=KEY[0];
332 assign LEDR[1]=KEY[1];
333 assign LEDR[2]=KEY[2];
334
335 LedMachine u1 (
336     .reset(!KEY[0]),
337     .clock(!KEY[2]),
338     .Key(!KEY[1]),
339     .Led(LEDG[0]) );
340
341 endmodule
```

Why is the clock the KEY[2]?

System Processing (195) Extra Info Info (51) Warning (144) Critical Warning Error Suppressed (6) Flag

Message: Location: Locate

For Help, press F1

Ln 333, Col 16 Idle

