

- a porta linear, circuito que permite a validação do sinal analógico em processamento por um sinal de controlo representando uma certa condição (trigger).
 - o conversor analógico-digital (ADC), que digitaliza as amplitudes dos sinais analógicos de entrada, atribuindo a cada sinal um canal de entre os 1024 existentes (caso da ADC de 10 bits: $2^{10} = 1024$). Se o ADC aceitar, p.ex., sinais na gama 0-10V (volt) de amplitude, um sinal de 3V será representado por um evento que incrementa o conteúdo do canal 307.
- A conversão analógico-digital costuma obter-se pelo método da descarga dum condensador em escala. O seu tempo de descarga é contado por um oscilador de alta frequência (~100 MHz). Assim, o tempo de conversão do ADC, para um sinal de amplitude máxima, é de dezenas de μs ($1024 \times 10 \mu\text{s}$).
- O ADC é, pois, um dispositivo lento. Para altas taxas de contagem (~ $10^5/\text{s}$), exibe tempo morto.

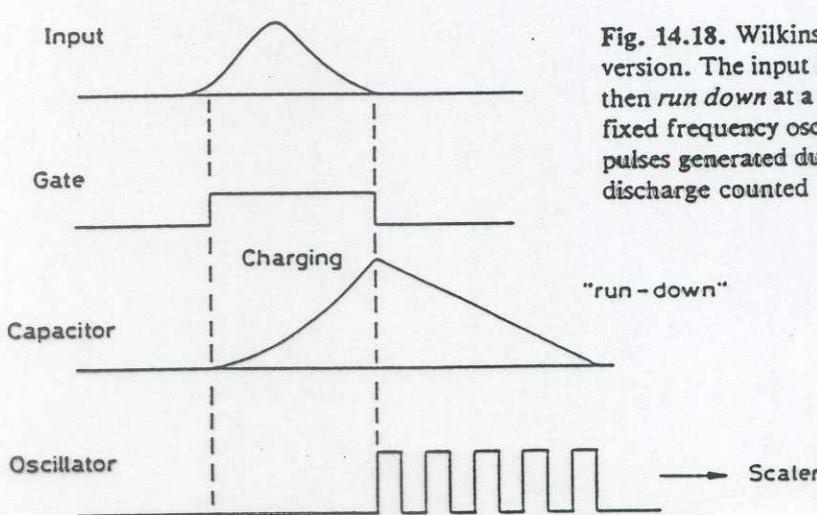


Fig. 14.18. Wilkinson method of analog-to-digital conversion. The input is used to charge a capacitor which is then run down at a constant current. At the same time, a fixed frequency oscillator is gated on and the number of pulses generated during the time it takes the capacitor to discharge counted